

Code: 19ES1101

I B.Tech - I Semester – Regular Examinations - December - 2019

**BASIC ELECTRICAL & ELECTRONICS
ENGINEERING**

(Common for IT, ECE, EEE)

Duration: 3 hours

Max. Marks: 70

-
- Note: 1. This question paper contains two Parts A and B.
2. Part-A contains 5 short answer questions. Each Question carries 2 Marks.
3. Part-B contains 5 essay questions with an internal choice from each unit. Each question carries 12 marks.
4. All parts of Question paper must be answered in one place.
-

PART – A

1. a) State Kirchhoff's laws.
- b) List the different types of losses occurred in a DC Machine.
- c) Draw the Torque-slip characteristics of a Three phase induction motor.
- d) Sketch V-I characteristics of practical diode in forward biased condition.
- e) Define the following:
 - i) Input offset voltage
 - ii) Slew rate.

PART – B

UNIT – I

2. a) Derive the expression for the equivalent resistance of 'n' number of resistances are connected in parallel. 6 M
- b) List the basic network elements. Write their volt-ampere relationship. 6 M

OR

3. a) State and Explain Superposition Theorem. 6 M
- b) Solve the equivalent resistance of resistances 4Ω , 5Ω , 5Ω are connected in parallel. 6 M

UNIT – II

4. a) Explain the constructional details of a DC machine with a neat diagram. 6 M
- b) Describe different methods of excitations in dc motors with relevant diagrams. 6 M

OR

5. a) Derive the torque equation of the DC motor. 6 M
- b) Draw the diagram of a 2 – point starter and explain the function of each component. 6 M

UNIT-III

6. a) Explain the necessity for conducting OC and SC tests on a single phase transformer and give its outcome. 6 M
- b) Explain the working principle of a Transformer with the help of neat sketch. 6 M

OR

7. a) Explain the working principle of Three-phase Induction motor. 6 M
- b) Derive the expression for torque developed by an Induction motor. 6 M

UNIT – IV

8. a) Explain with a neat diagram the operation of a Full wave rectifier and also draw its output wave forms. 6 M
- b) Draw and Explain the V-I characteristics of a Zener diode. 6 M

OR

9. a) Explain the formulation of depletion region in a PN junction. 6 M
- b) Compare NMOS with PMOS. 6 M

UNIT – V

10. a) Describe the inverting op-amp with circuit diagram and derive the necessary expressions. 6 M
- b) Explain the function of all the basic building blocks of an op-amp. 6 M

OR

11. a) Explain the characteristics of op-amp. 6 M
- b) Explain the closed loop and open loop operation of an op-amp. 6 M