

Code: EC1T6

**I B.Tech - I Semester – Regular / Supplementary Examinations
November 2018**

**INTRODUCTION TO ELECTRICAL CIRCUITS
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22 M

1.

- a) Two resistors are connected in series across a 24 V supply and a current of 3 A flows in the circuit. If one of the resistors has a resistance of 2 Ω . Determine the value of the other resistor.
- b) Capacitances of 1 μF , 3 μF , 5 μF and 6 μF are connected in parallel to a direct voltage supply of 100 V. Determine
i) the equivalent circuit capacitance, ii) the total charge.
- c) An 8 H inductor has a current of 3 A flowing through it. How much energy is stored in the magnetic field of the inductor?
- d) A coil of resistance 5 Ω and inductance 120 mH in series with a 100 μF capacitor, is connected to a 300 V, 50 Hz supply. Calculate i) the current flowing, ii) the phase difference between the supply voltage and current.
- e) A 20 Ω resistor is connected in parallel with an inductance of 2.387 mH across a 60 V, 1 kHz supply. Calculate i) the current in each branch, ii) the supply current.


- f) Obtain the admittance of RL parallel resonance.
- g) A 12 V battery is connected in a circuit having three series-connected resistors having resistances of 4 Ω , 9 Ω and 11 Ω . Determine the current flowing through, and the p.d. across the 9 Ω resistor. Find also the power dissipated in the 11 Ω resistor.
- h) Write the impedance of an RL series circuit and write its phasor diagram.
- i) Obtain the RLC series circuit resonance frequency with reactance diagram.
- j) Define form factor and peak factor of an ac periodic wave form.
- k) Define magnetic flux and magnetic flux density.

PART – B

Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

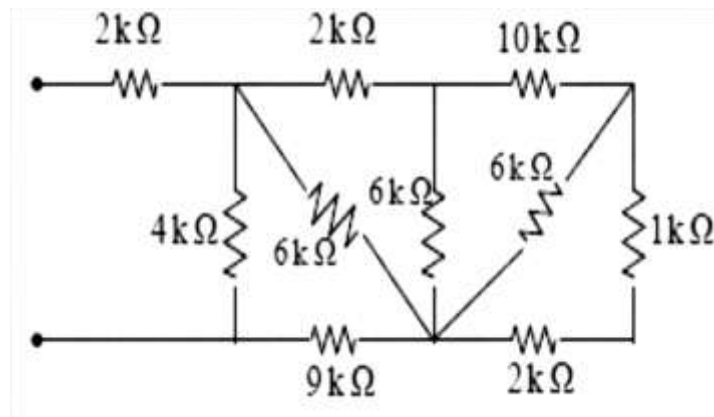
2. a) Find equivalent resistance for the circuit shown below



8 M

- b) Find the power associated with the 6 V source for the circuit shown below

8 M

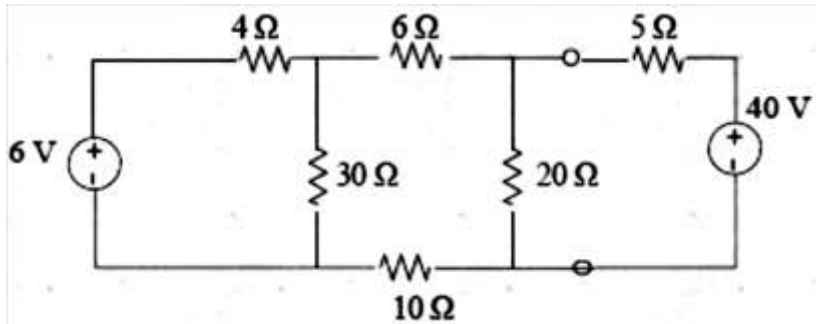


3. a) Explain the phase representation of alternating voltage and give the significance of 'j' operator.

6 M

- b) Determine the average, rms values and form factor and peak factors for a rectangular waveform given for one cycle for a period.

10 M

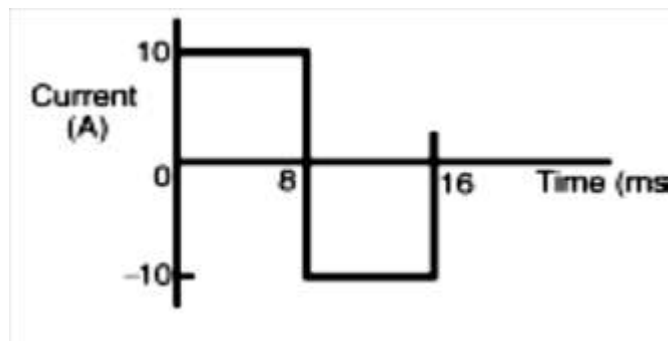

4. a) Obtain coefficient of coupling K between two coils of inductances connected in series.

8 M

- b) The energy stored in the magnetic field of an inductor is 80 J when the current flowing in the inductor is 2 A. Calculate the inductance of the coil.

8 M

5. a) A coil of resistance 5Ω and inductance of 120mH and a capacitor of $20\mu\text{F}$ is connected to a 230 V , 50Hz supply. Calculate the current flowing, phase difference between supply voltage and current, voltage across the coil and the voltage across the capacitor. 8 M
- b) Obtain the impedance of a series RLC circuit connected to an ac supply. Draw the voltage and impedance diagrams and explain. 8 M
6. a) The power taken by an inductive circuit when connected to a 120 V , 50 Hz supply is 400 W and the current is 8 A . Calculate: i) the resistance, ii) the impedance, iii) the reactance, iv) the power factor, and v) the phase angle between voltage and current. 8 M
- b) A coil of inductance 80 mH and negligible resistance is connected in series with a capacitance of $0.25 \mu\text{F}$ and a resistor of resistance 12.5Ω across a 100 V , variable frequency supply. Determine: i) the resonant frequency, and ii) the current at resonance. How many times greater than the supply voltage is the voltage across the reactances at resonance? 8 M