

Code: 20ES1101

**I B.Tech - I Semester – Regular / Supplementary  
Examinations – APRIL 2022**

**BASIC ELECTRICAL & ELECTRONICS  
ENGINEERING  
(Common to CIVIL, CSE, IT)**

Duration: 3 hours

Max. Marks: 70

Note: 1. This paper contains questions from 5 units of Syllabus. Each unit carries 14 marks and have an internal choice of Questions.  
2. All parts of Question must be answered in one place.

**UNIT – I**

1. a) Determine the value of resistance between the terminals A-B ( $R_{AB}$ ) for the network shown in Figure.1? 7 M

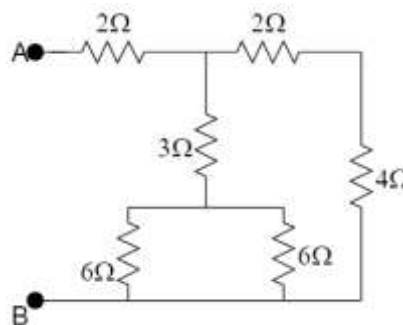


Figure.1

- b) Apply the superposition theorem to the circuit shown in Figure.2 to find the current flowing through 6 Ω resistor. 7 M

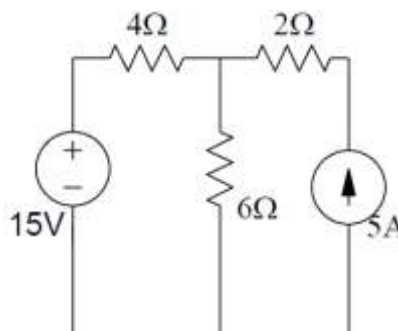


Figure. 2

OR

2. a) Apply the mesh analysis on the circuit shown in Figure.3 and find the current  $I$  flowing in the  $2\Omega$  resistor. 7 M

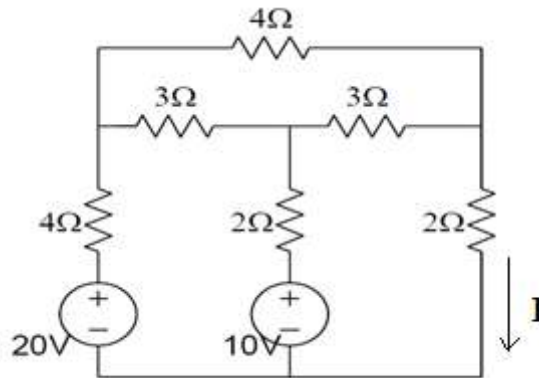


Figure.3

- b) Simplify the circuit shown in Figure. 4 using the Norton's theorem and determine the current through  $4\Omega$  resistor. 7 M

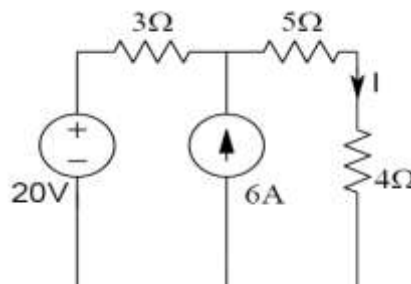


Figure. 4

### UNIT – II

3. a) (i) Draw the constructional features of a DC machine and give their functions. 5 M  
(ii) Why is commutator employed in DC machines? 2 M
- b) Derive emf equation of a DC generator (or DC machine). 7 M

OR

4. a) Explain the working principle of a DC motor with appropriate sketches. 7 M
- b) Derive an expression for the speed of a DC motor in terms of back emf and flux per pole. 7 M

### **UNIT-III**

5. a) Develop an expression for the emf induced in a transformer winding. Show that the emf induced per turn in primary is equal to the emf per turn in secondary. 7 M
- b) Determine the efficiency of a single-phase transformer by utilizing the open circuit and short circuit tests. Draw the circuit diagrams for each test and mention uses of these tests. 7 M

OR

6. a) Illustrate the constructional details of single phase transformer. 7 M
- b) Explain the working principle of a three phase induction motor with relevant sketches. 7 M

### **UNIT – IV**

7. a) Draw the circuit diagram of Half-wave rectifier and derive the expressions for average value and R.M.S value. 7 M
- b) Generalize the working of Zener diode as a voltage regulator. 7 M

OR

8. a) Explain the working of p-n junction diode in forward and reverse bias conditions. Draw its V-I characteristics. 7 M
- b) What is the use of filter capacitor? With suitable example, differentiate the operation and output of rectifiers with and without filter capacitor. 7 M

### UNIT – V

9. a) Obtain the expression for gain of the non-inverting configuration of op-amp. 7 M
- b) Distinguish the different characteristics of ideal and practical op-amp. 7 M

OR

10. a) What is a voltage follower? Explain its operation with necessary diagrams and expressions. 7 M
- b) Explain how an op-amp can be used as an inverting amplifier, non-inverting amplifier? Derive expressions for output voltages. 7 M