

Code: EC3T4

II B.Tech - I Semester – Regular Examinations – December 2015

**NETWORK ANALYSIS AND SYNTHESIS
(ELECTRONICS AND COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A


Answer *all* the questions. All questions carry equal marks
11x 2 = 22 M

1. a) What is a Supermesh? Write the steps involved to write a supermesh equation for a given network.
- b) State Tellegen's Theorem.
- c) What are planar and non-planar graphs?
- d) What is the condition for symmetry in ABCD parameters?
- e) Write the properties of an incidence matrix.
- f) Write the solution of the current for a DC response of an R-C series circuit.
- g) What do you understand by transient and steady state parts of a response? How they can be identified in a general solution?
- h) Write the expression of ABCD parameters in terms of Z-parameters.
- i) Write the necessary conditions for driving point function.
- j) What is a network function? When do you say that the network function is said to be stable?
- k) What are the properties of Hurwitz polynomials?


PART – B

Answer any **THREE** questions. All questions carry equal marks. 3 x 16 = 48 M


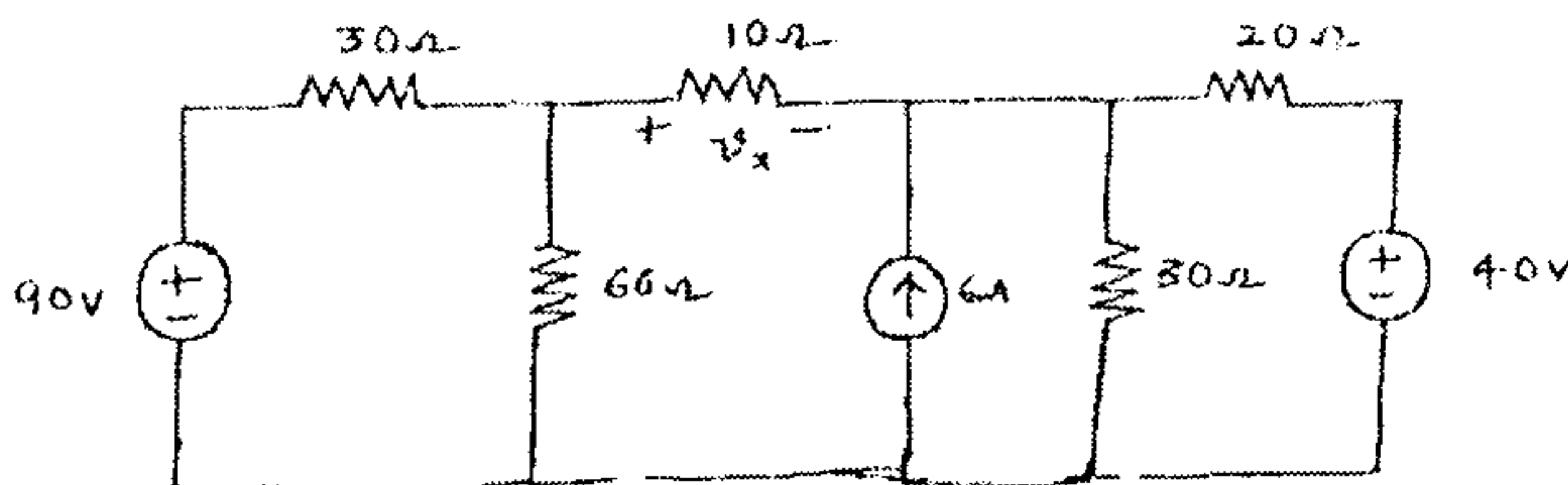
2. a) Use Superposition theorem to obtain v_x , in the circuit shown below. 8 M



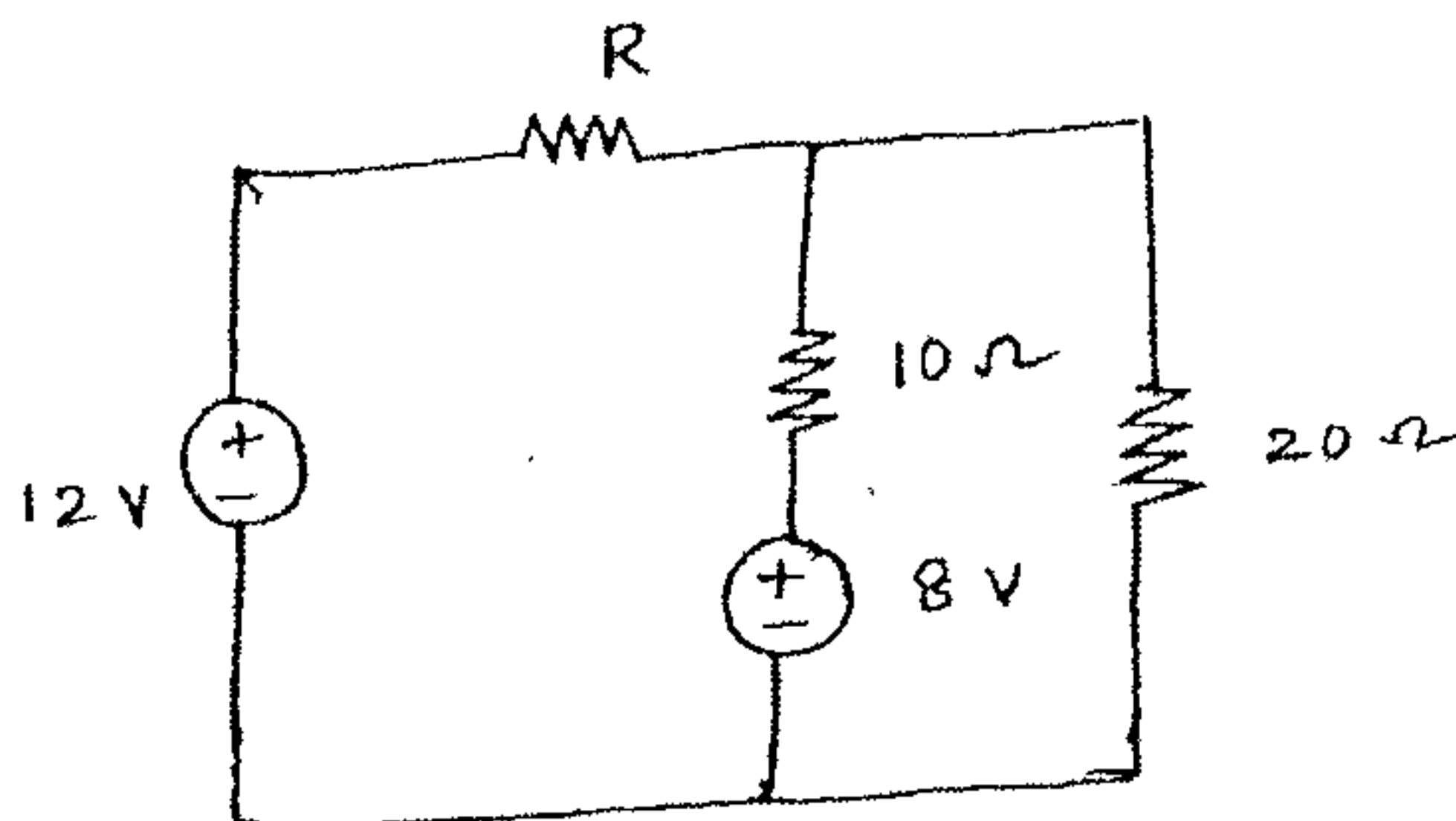
b) Compute the value of R that results in maximum power transfer to the $10\ \Omega$ resistor for the circuit shown below. Find also the maximum power. 8 M



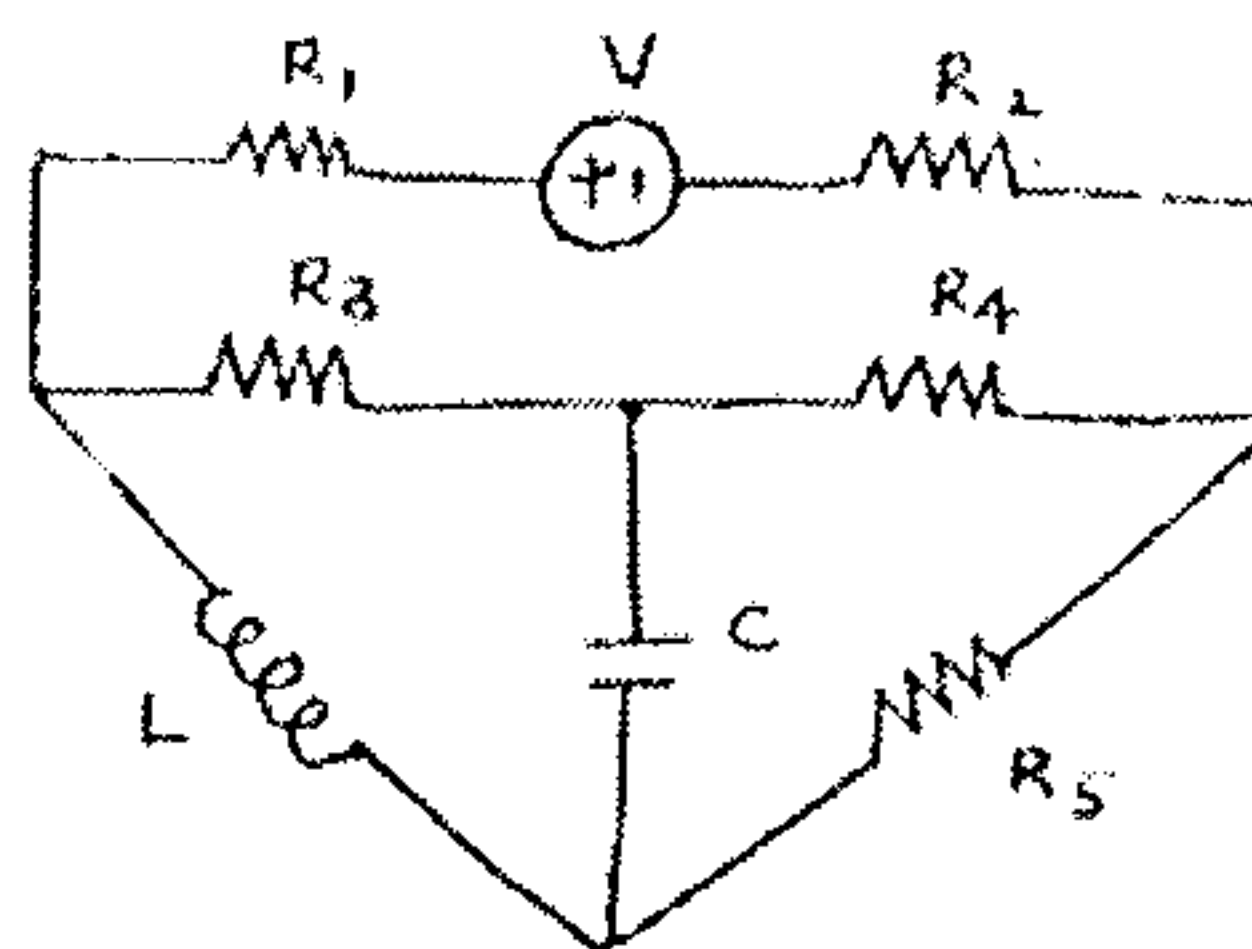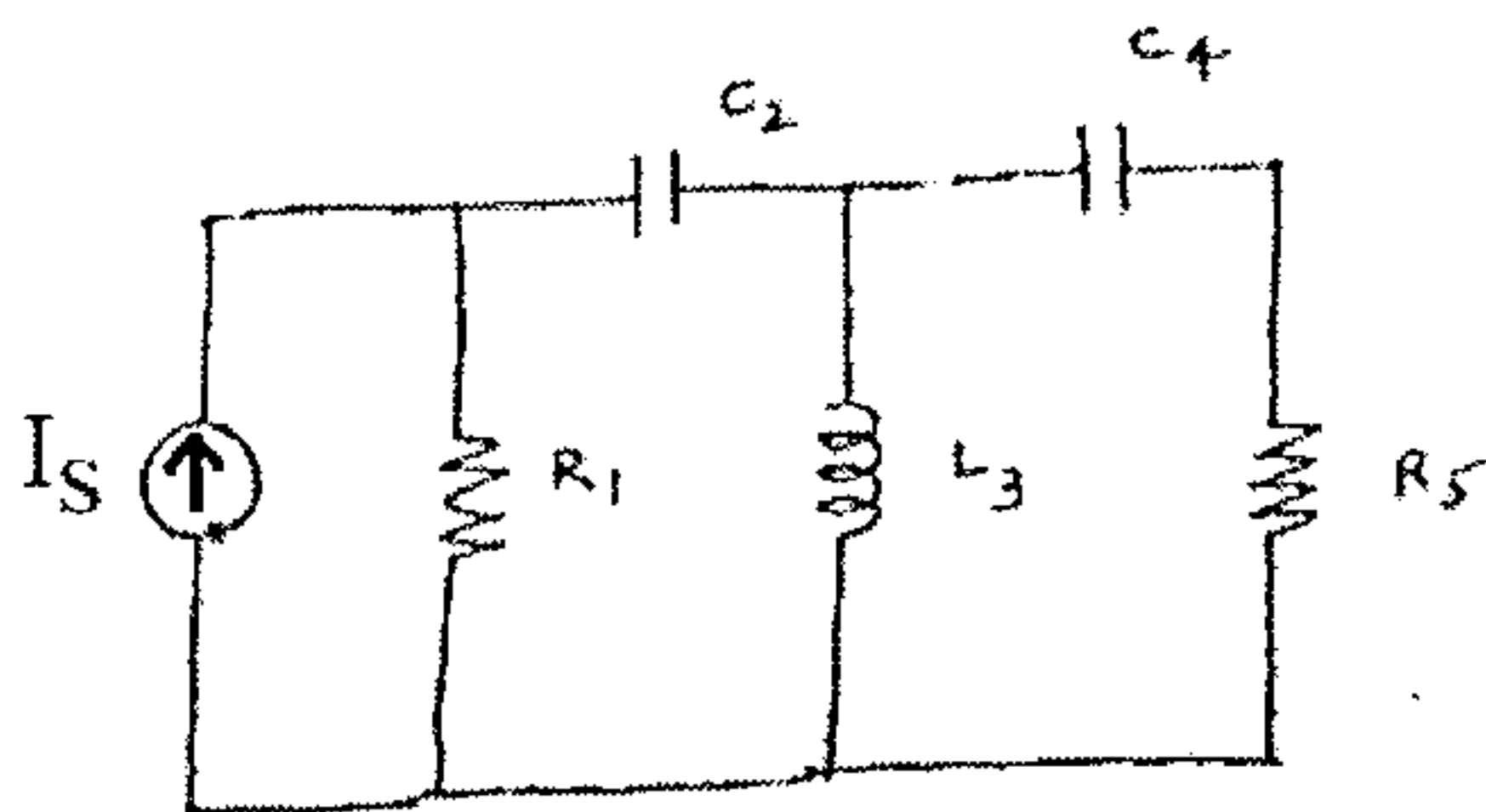
3. a) Draw the dual for the following networks. 8 M



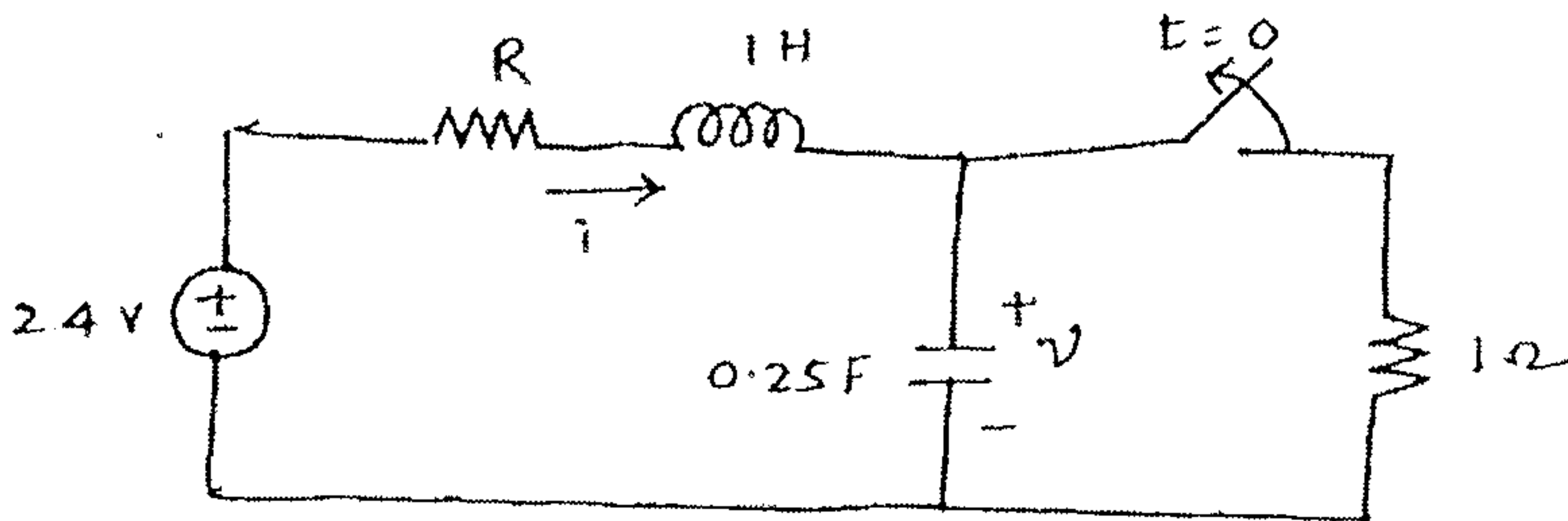
- b) For the circuit shown below, find $v(t)$ and $i(t)$ for $t > 0$.
 Consider these cases: $R=5\Omega$, $R=4\Omega$ and $R=1\Omega$. 8 M



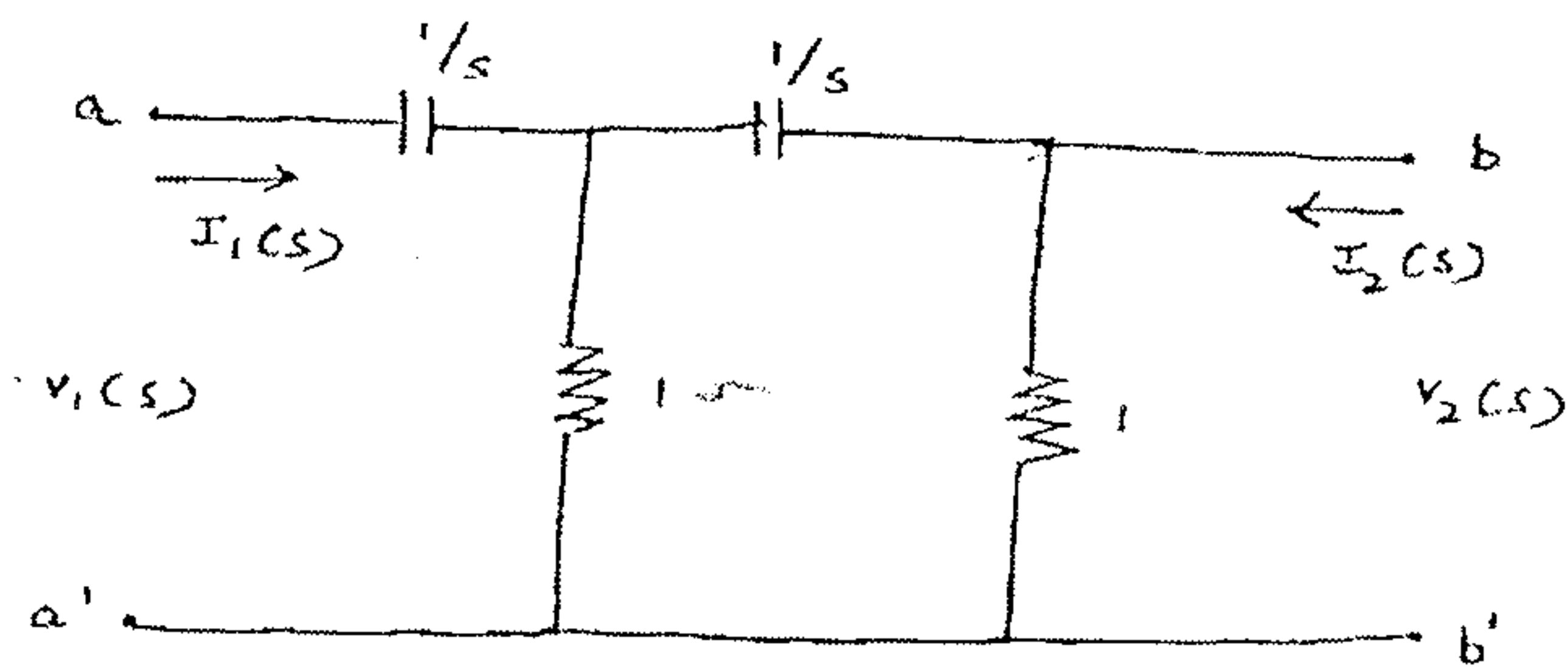4. a) Find the Z parameters of the RC ladder network shown in circuit below. 8 M




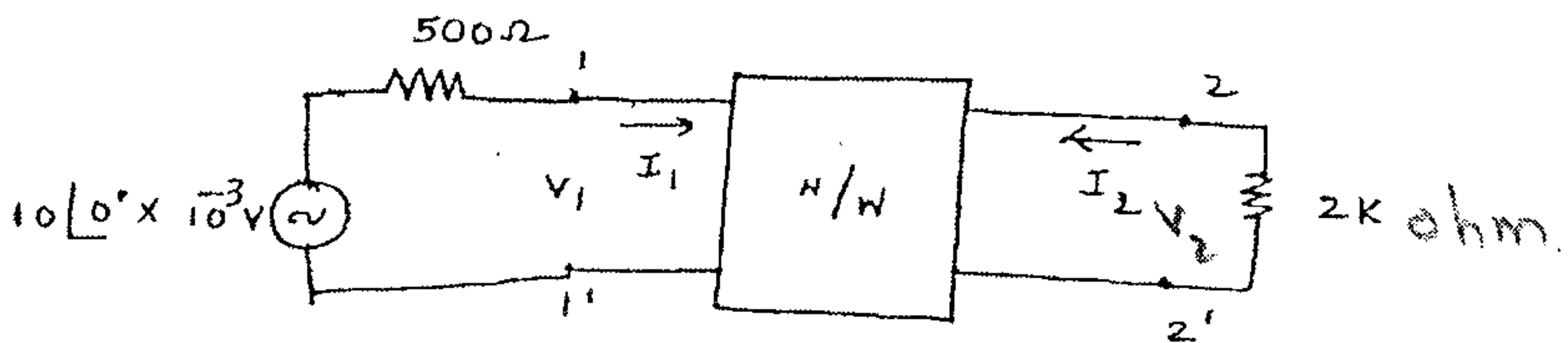- b) The hybrid parameters of a two port network shown in figure are $h_{11}=0.003\Omega$; $h_{12}=h_{21}=100$; $h_{22}=50\mu \text{ mho}$. Find V_2 and Z parameters of the network. 8 M




5. a) For the network shown, determine the transform impedance $Z(s)$.

8 M

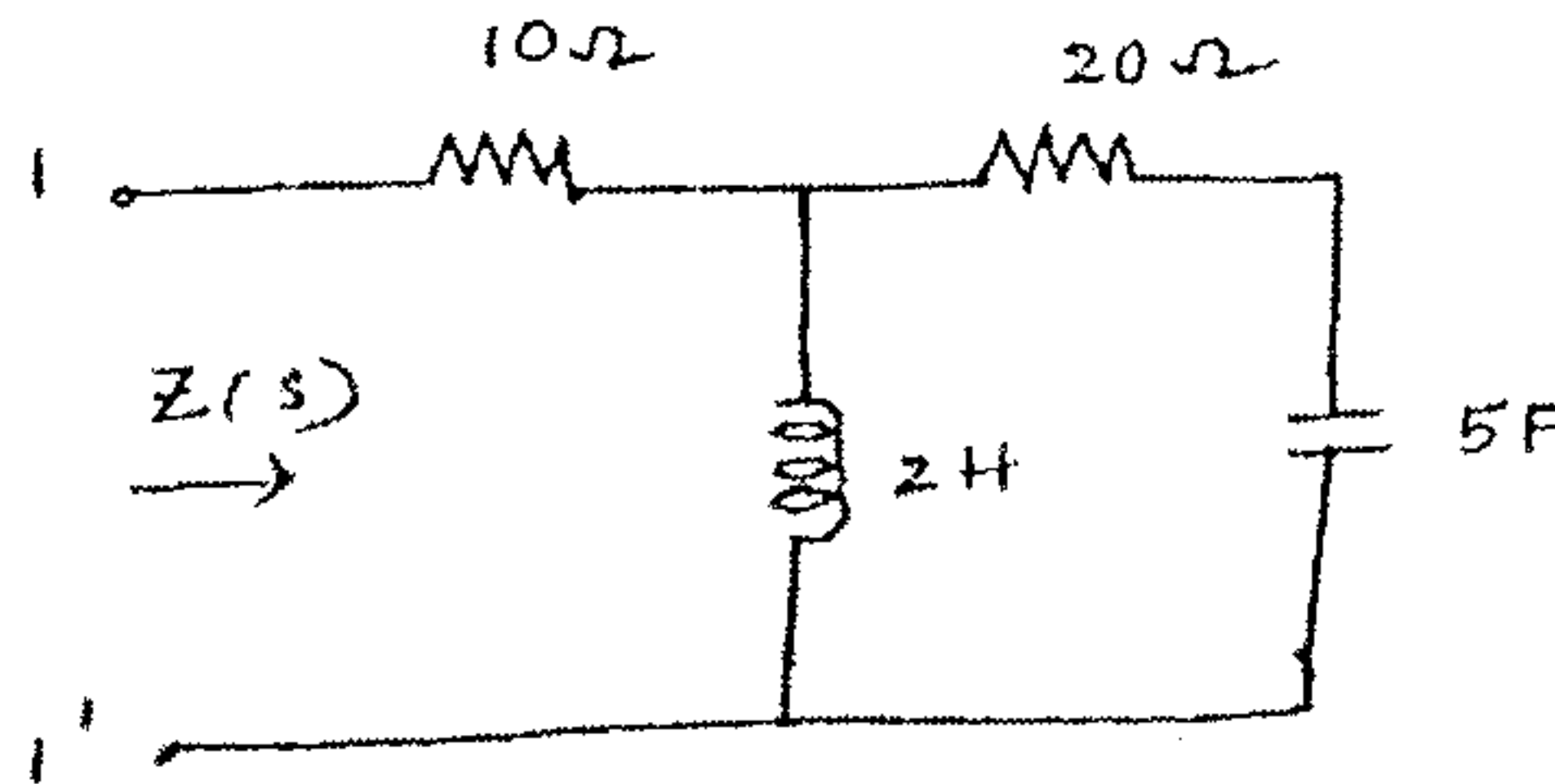

- b) Find the driving point impedance of the network shown in the figure. Also find the zeros and poles of the network and locate them in the s -plane.

8 M

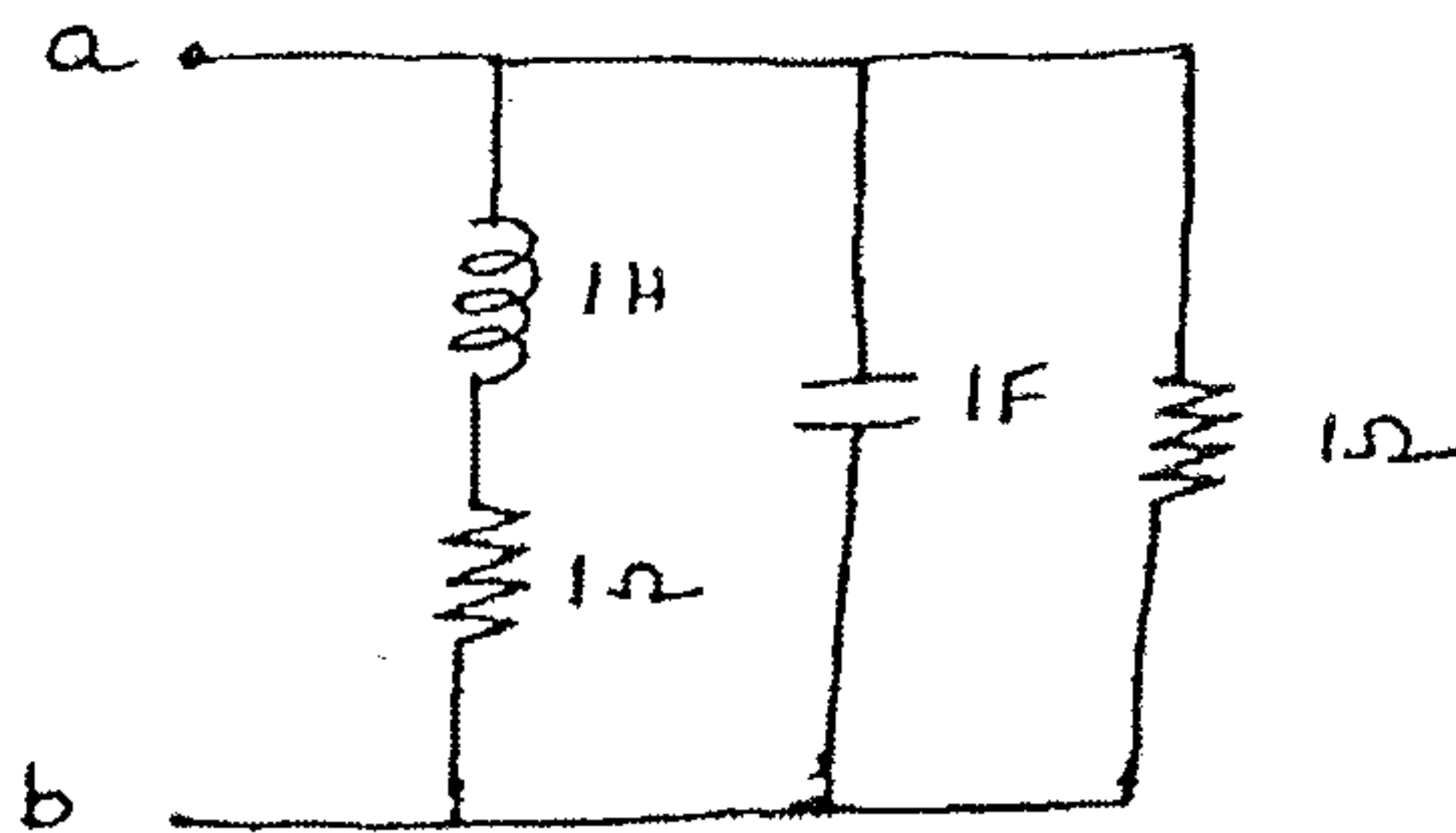

6. a) What are the properties of positive real functions? Explain with examples.

8 M

- b) Realize the following function having impedance function

$$z(s) = \frac{s^2 + 4s + 40}{s(s + 10)}$$

8 M