

Code: EC3T4

**II B.Tech - I Semester – Regular/Supplementary Examinations  
November - 2018**

**NETWORK ANALYSIS AND SYNTHESIS  
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

**PART – A**

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) State Superposition Theorem. Explain.
- b) What is significance of Maximum power transfer Theorem?
- c) State Millman's Theorem.
- d) Define Incidence matrix and Cutset matrix.
- e) What is time constant of series RL circuit? Explain its significance.
- f) What are Z-parameters?
- g) What is relation between Z and Y parameters?
- h) What is significance of poles and zeros?
- i) Define Transfer function and state its importance.
- j) Mention the two properties of Positive Real function.
- k) What is the difference between network analysis and synthesis?


## PART – B

Answer any **THREE** questions. All questions carry equal marks.

3 x 16 = 48 M


2. a) Determine the current in the  $2\Omega$  resistor for the circuit shown below, by using nodal analysis.

8 M

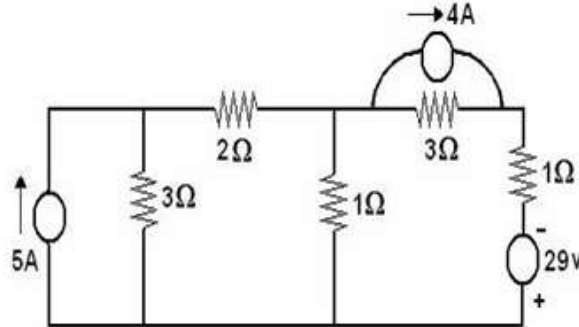


- b) Find Thevenin's equivalent of the network shown below at X-Y terminals.

8 M

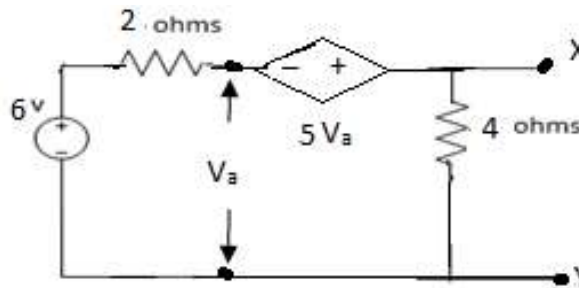


3. a) Find the power dissipated by  $2\Omega$  resistor by constructing tie-set and cut-set matrices.


8 M

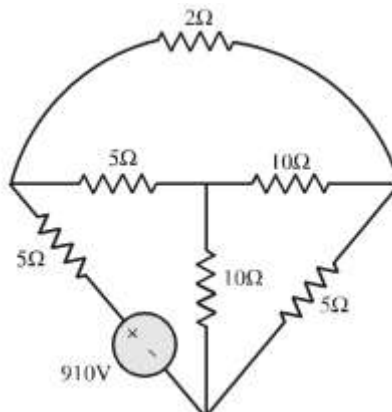

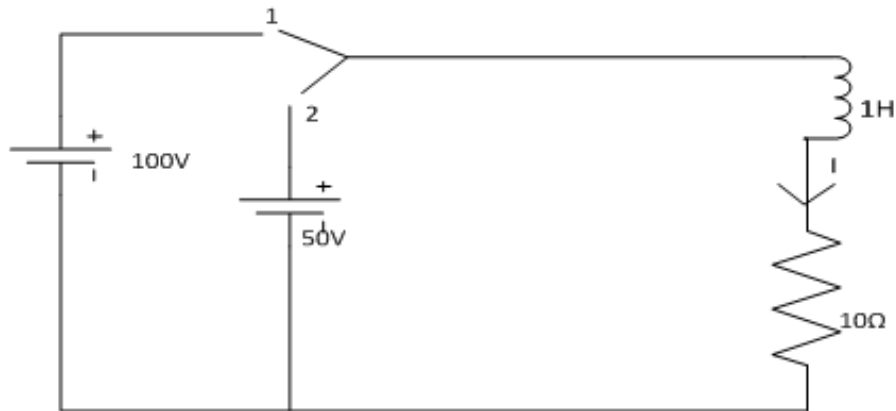
b) The switch is in position 1 for long time and moved to position 2 at  $t=0$ , find current  $i$ . 8 M



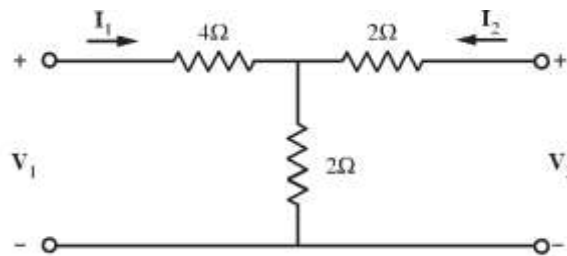4. a) Find the h and ABCD parameters of the two-port network shown below. 10 M



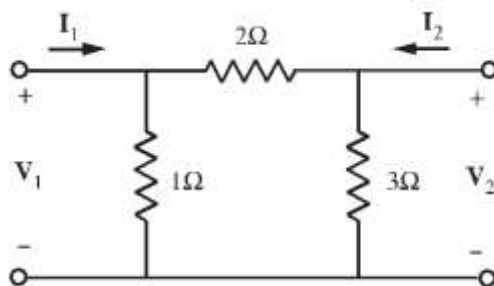b) Find the y-parameters of the two-port network shown below. 6 M



5. a) What are necessary conditions for a driving point function? 6 M

b) Draw the pole zero diagram for the given function

$$V(s) = \frac{4(s+2)s}{(s+1)(s+3)} \quad \text{and hence obtain } V(t). \quad 10 \text{ M}$$

6. a) A driving point function is given by  $F(S) = \frac{S^2 + 6S + 8}{S^2 + 4S + 3}$ .

Show that the function can be realized in both RC & RL forms. 10 M

b) For the driving point function  $\frac{(S + 2)(S + 1)}{S(S + 3)}$ . Design a network by choosing the elements on your own. 6 M