

Code: 20EC3304

**II B.Tech - I Semester –Regular / Supplementary Examinations  
DECEMBER 2022**

**NETWORK THEORY AND ANALYSIS  
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

Note: 1. This paper contains questions from 5 units of Syllabus. Each unit carries 14 marks and have an internal choice of Questions.

2. All parts of Question must be answered in one place.

BL – Blooms Level


CO – Course Outcome

			BL	CO	Max. Marks
<b>UNIT-I</b>					
1	a)	Analyze a series RLC excited by sinusoidal voltage to obtain the phase relation between applied voltage and current.	L4	CO3	6 M
	b)	The voltage and a current in a circuit are given $v=150\angle 30^\circ\text{V}$ , $I=2\angle -15^\circ\text{A}$ . If the circuits works at 50Hz supply, solve for impedance, resistance, reactance, power factor and power consumed.	L3	CO2	8 M
<b>OR</b>					
2	a)	Explain the following: (i) Average Voltage (ii) Power factor (iii) Form factor (iv) Apparent power (v) Reactive power (vi) Power triangle	L2	CO1	6 M
	b)	A sine wave generator supplies a 500 Hz, 10 $V_{\text{rms}}$ to a $2\text{k}\Omega$ resistor in series with a $0.1\mu\text{F}$ capacitor. Solve for parameters, the total impedance $Z$ , current $I$ , phase angle $\theta$ ,	L3	CO3	8 M

capacitive voltage  $V_c$  and resistive voltage  $V_R$ .

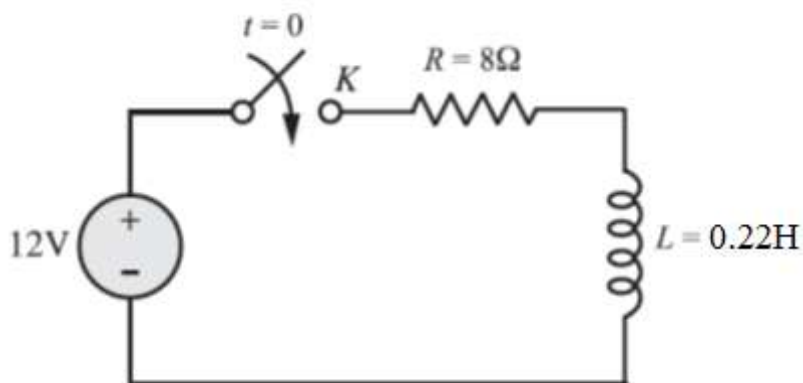
### UNIT-II

3 a) In the given network, k is closed at  $t = 0$  with zero current in the inductor. Find the values of  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t=0^+$  if  $R=8\Omega$ , and  $L= 0.22H$ .



L3 CO2 7 M

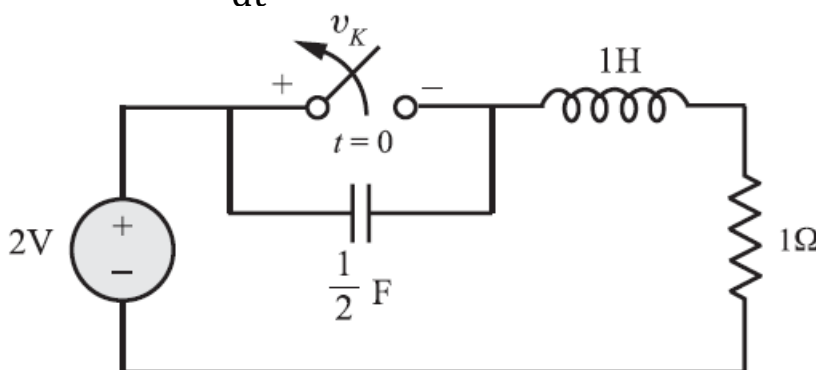
b) The circuit shown in Fig. is in steady state with switch K closed. At  $t=0$ , the switch is opened. Determine the voltage across the switch,  $v_k$ ,  $\frac{dv_k}{dt}$ , at  $t= 0^+$ .




L3 CO2 7 M
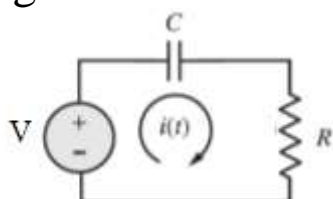
### OR



4 a) Consider the RC circuit shown in Fig . Find  $i(t)$  by assuming circuit is initially relaxed.



L4 CO4 7 M

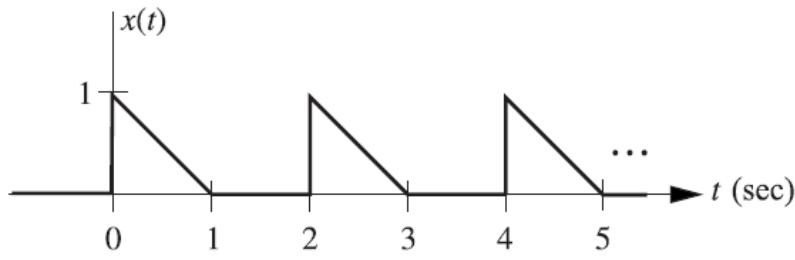
	<p>b) Find the Laplace transform of the periodic signal <math>x(t)</math> shown in Fig.</p> 	L4	CO4	7 M
--	--	----	-----	-----

### UNIT-III

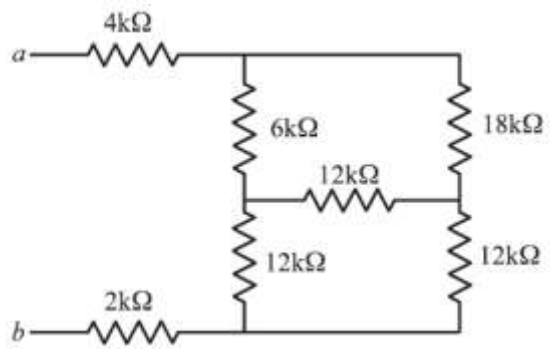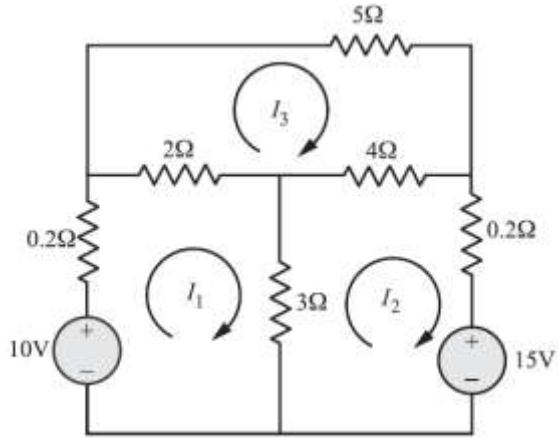
5	<p>a) Find the value of resistance between the terminals a-b of the network shown in Fig.</p> 	L3	CO2	7 M
	<p>b) For the electrical network shown in Fig., determine the loop currents and all branch currents.</p> 	L3	CO2	7 M

**OR**

6	<p>a) Use superposition to find <math>i_0</math> in the circuit shown in Fig.</p>	L4	CO3	7 M
---	---	----	-----	-----

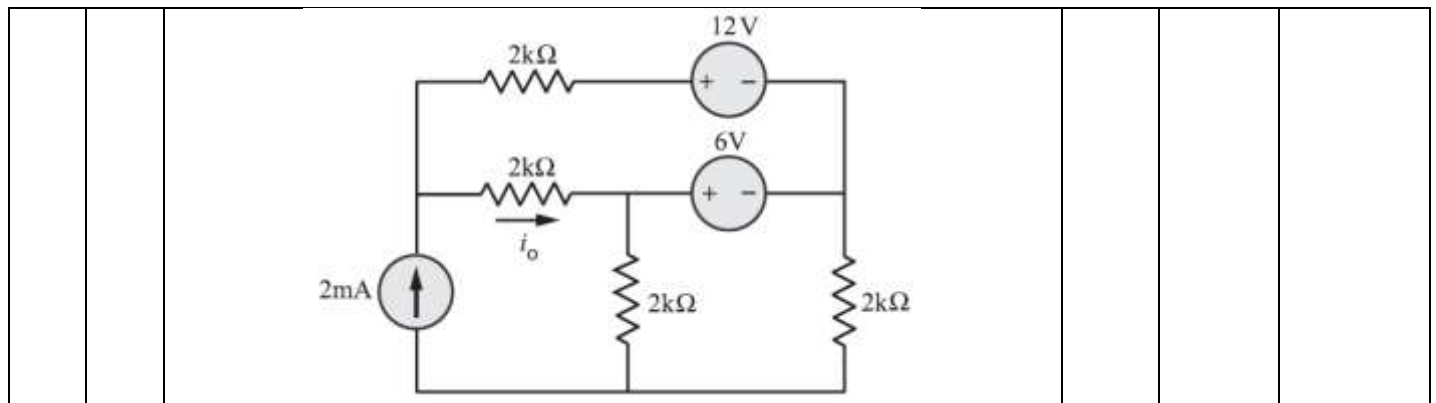

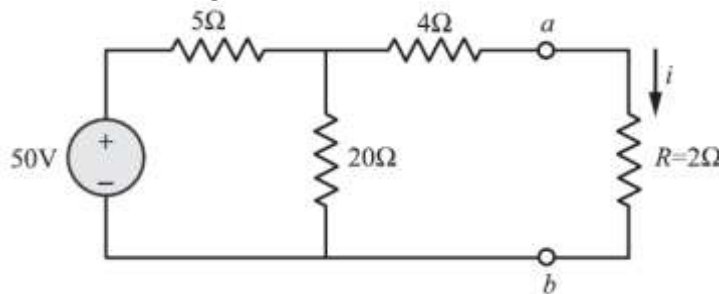
b) Using the Thevenin's theorem, find the current  $i$  through  $R = 2\Omega$ .



L3 CO2 7 M
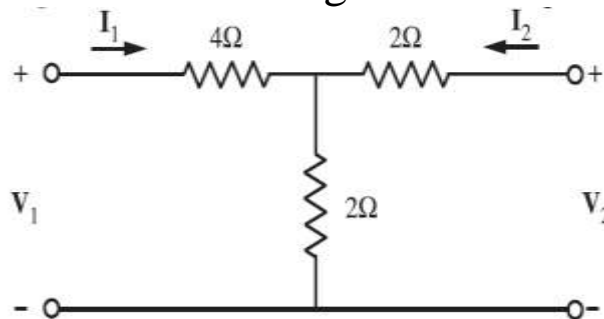
### UNIT-IV


7 a) Determine the admittance parameters of the T network shown in Fig.



L4 CO3 7 M

b) Find the  $z$  parameters of the circuit shown in the fig. Then compute the current in a  $4\Omega$  load if a  $24\angle 0^\circ$  V source is connected at the input port.

L4 CO3 7 M

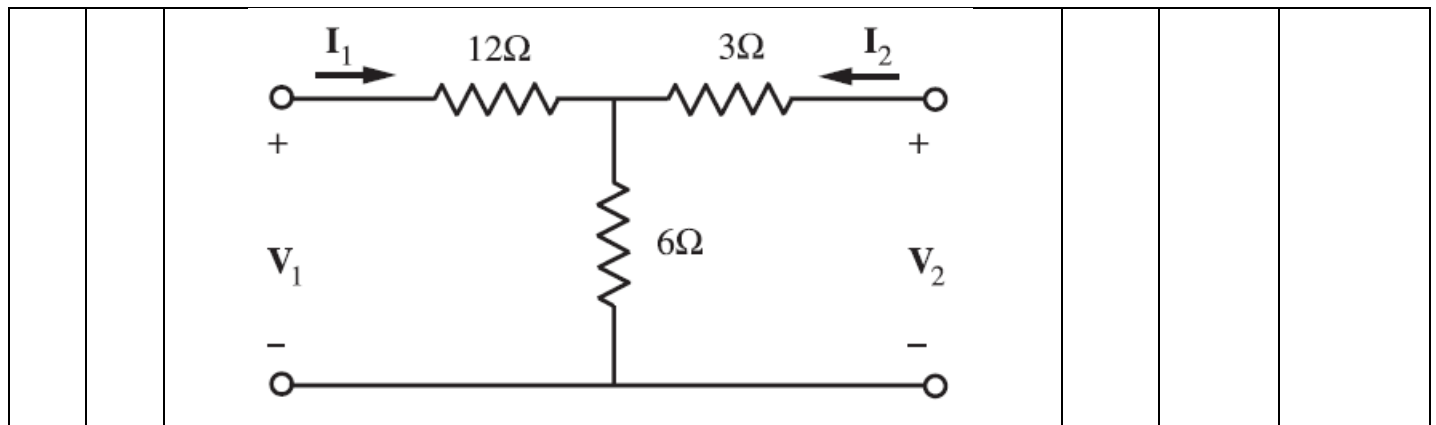





**OR**

8	a)	<p>Find the hybrid parameters for the two-port network shown in Fig.</p>	L4	CO3	7 M
---	----	--	----	-----	-----

	b)	<p>Find the transmission parameters for the network shown in Fig.</p>	L4	CO3	7 M
--	----	---	----	-----	-----

**UNIT-V**

9	a)	<p>For the circuit shown in figure find the following (i) The resonant frequency <math>f_o</math> (ii) Quality factor <math>Q</math> (iii) <math>f_{c1}</math>, <math>f_{c2}</math> (iv) Bandwidth <math>B</math></p>	L4	CO4	7 M
---	----	---	----	-----	-----

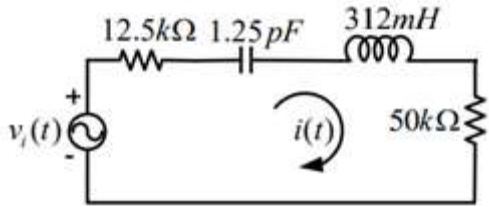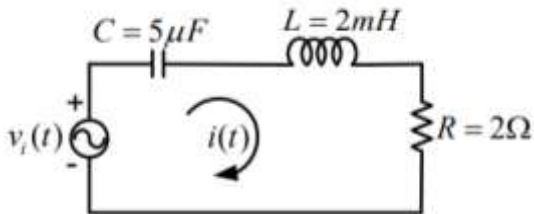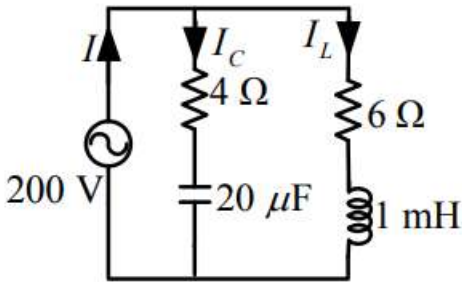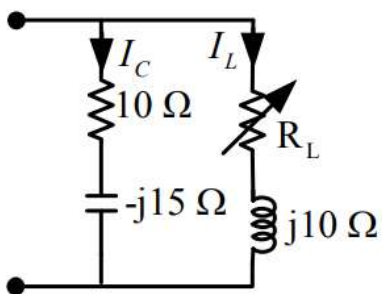					
	b)	<p>For the circuit shown in figure find the resonant frequency, quality factor and bandwidth for the circuit. Determine the change in Q and the bandwidth if R is changed from <math>R = 2 \Omega</math> to <math>R = 0.4 \Omega</math></p> 	L4	CO4	7 M
<b>OR</b>					
10	a)	<p>For the circuit as shown in Fig. find the resonant frequency and the corresponding current in each branch.</p> 	L4	CO4	7 M
	b)	<p>Find the value of <math>R_L</math> for which the circuit as shown in Fig. is resonant.</p> 	L4	CO4	7 M