

Code: 20EC3302

**II B.Tech - I Semester – Regular / Supplementary Examinations
DECEMBER 2023**

**DIGITAL LOGIC DESIGN
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

Note: 1. This paper contains questions from 5 units of Syllabus. Each unit carries 14 marks and have an internal choice of Questions.
2. All parts of Question must be answered in one place.

BL – Blooms Level


CO – Course Outcome

			BL	CO	Max. Marks
UNIT-I					
1	a)	Convert the $(101101.1101)_2$ number into Decimal, Hexadecimal and octal form.	L2	CO1	7 M
	b)	State and Prove De Morgan's Theorems using truth table.	L2	CO1	7 M
OR					
2	a)	Explain about any four binary codes.	L2	CO1	7 M
	b)	The Hamming code 101101101 is received. Correct it if any errors are available. Where 4 parity bits are used.	L2	CO1	7 M
UNIT-II					
3	a)	Simplify the following Boolean function for minimal SOP form using K-Map method. $F(A, B, C, D) = \sum m(0,1,2,3,5,7,8,9,11,14)$	L3	CO2	7 M

	b)	Find the dual and complement for the following function $F=ABC+A'B'C'+AB'C'+A'BC+AB'C$	L3	CO2	7 M
OR					
4	a)	Convert $F(X, Y, Z) = X'Y + X'Z + YZ$ into canonical SOP form.	L2	CO2	6 M
	b)	Simplify the following Boolean equation using K-map. $F(W,X,Y,Z)=\sum m(0,7,8,9,10,12) + \sum d(2,5,13)$. Implement the simplified expression using NAND Gates.	L3	CO2	8 M
UNIT-III					
5	a)	Design 3 to 8 decoder using 2 to 4 decoders and OR gate.	L4	CO3	7 M
	b)	Design 16x1 Mux using 4x1 Multiplexers.	L4	CO3	7 M
OR					
6	a)	Design 4-bit Binary Adder/Subtractor circuit with neat sketches.	L4	CO3	8 M
	b)	Implement the function $F(A, B, C) = \sum m(1, 3, 5, 6)$ using 2x1 Mux.	L3	CO3	6 M
UNIT-IV					
7		Summarize the SR, JK, D & T flip-flops with its characteristic and Excitation tables.	L2	CO4	14 M
OR					
8	a)	Explain about SIPO shift Register with neat sketches.	L2	CO4	7 M
	b)	Outline about the steps in synchronous counters design.	L2	CO4	7 M

UNIT-V

9	a)	Explain about the Analysis of clocked sequential circuits with an Example.	L4	CO5	7 M
	b)	Design the following synchronous sequential circuit using T Flip-Flops.	L2	CO5	7 M

 

OR

10		<table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th rowspan="2">PS</th> <th colspan="2">NS, Z</th> </tr> <tr> <th>X=0</th> <th>X=1</th> </tr> </thead> <tbody> <tr><td>A</td><td>B,1</td><td>H,1</td></tr> <tr><td>B</td><td>F,1</td><td>D,1</td></tr> <tr><td>C</td><td>D,0</td><td>E,1</td></tr> <tr><td>D</td><td>C,0</td><td>F,1</td></tr> <tr><td>E</td><td>D,1</td><td>E,1</td></tr> <tr><td>F</td><td>C,1</td><td>E,1</td></tr> <tr><td>G</td><td>C,1</td><td>D,1</td></tr> <tr><td>H</td><td>C,0</td><td>A,1</td></tr> </tbody> </table>	PS	NS, Z		X=0	X=1	A	B,1	H,1	B	F,1	D,1	C	D,0	E,1	D	C,0	F,1	E	D,1	E,1	F	C,1	E,1	G	C,1	D,1	H	C,0	A,1	L4	CO5	14 M
PS	NS, Z																																	
	X=0	X=1																																
A	B,1	H,1																																
B	F,1	D,1																																
C	D,0	E,1																																
D	C,0	F,1																																
E	D,1	E,1																																
F	C,1	E,1																																
G	C,1	D,1																																
H	C,0	A,1																																
	<p>For the above state table obtain the following</p> <ol style="list-style-type: none"> i. Draw the corresponding state diagram ii. Tabulate the reduced state table iii. Draw the state diagram corresponding to the reduced state table. 																																	