

Code: 20EC3304

**II B.Tech - I Semester –Regular / Supplementary Examinations
DECEMBER 2023**

**NETWORK THEORY AND ANALYSIS
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours


Max. Marks: 70

Note: 1. This paper contains questions from 5 units of Syllabus. Each unit carries 14 marks and have an internal choice of Questions.

2. All parts of Question must be answered in one place.

BL – Blooms Level

CO – Course Outcome

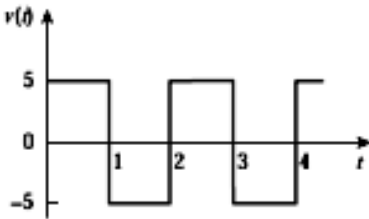			BL	CO	Max. Marks
UNIT-I					
1	a)	Calculate the RMS value of the voltage waveform shown below. 	L2	CO1	7 M
	b)	Compare phasor relationships for R, L and C circuit components.	L2	CO1	7 M
OR					
2	a)	Explain the concept of phasors with suitable example.	L2	CO1	7 M
	b)	Define power factor. Why power factor is important in circuits?	L2	CO1	7 M
UNIT-II					
3	a)	Derive the transient response of series RC-circuit with DC excitation.	L3	CO2	7 M

	b)	A series RL circuit with $R=30\Omega$ and $L= 15H$ has a constant voltage $V=60$ volts applied at $t=0$. Determine the current in the circuit, voltage across resistor and voltage across inductor.	L3	CO2	7 M
--	----	--	----	-----	-----

OR


4	a)	Derive the transient response of series RL circuit with DC excitation.	L3	CO2	7 M
	b)	Write a short note on transient analysis of a circuit.	L2	CO2	7 M

UNIT-III

5	a)	Determine the current in 10Ω resistor for the following network by using nodal analysis.	L4	CO3	7 M
	b)	State and prove superposition theorem.	L2	CO3	7 M

OR


6	a)	For the given circuit, determine the current flowing through 10Ω resistor using Norton's theorem.	L4	CO3	7 M

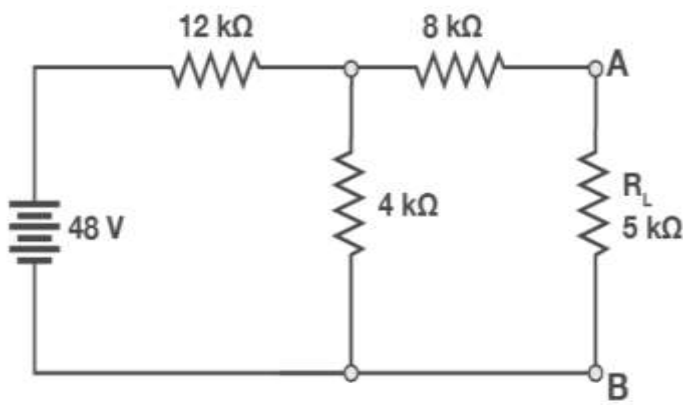	<p>b) Find V_{TH}, R_{TH} and the load current I_L flowing through and load voltage V_L across the load resistor in the circuit below using Thevenin's Theorem.</p> 	L4	CO3	7 M
--	--	----	-----	-----

UNIT-IV

7	<p>a) Derive the relation between ABCD and Z-parameters.</p>	L3	CO2	7 M
	<p>b) The Z-parameters of a two-port network are $Z_{11} = 10\Omega$, $Z_{22} = 15\Omega$, $Z_{12} = 5\Omega$ and $Z_{21} = 5\Omega$. Find ABCD parameters.</p>	L2	CO1	7 M

OR

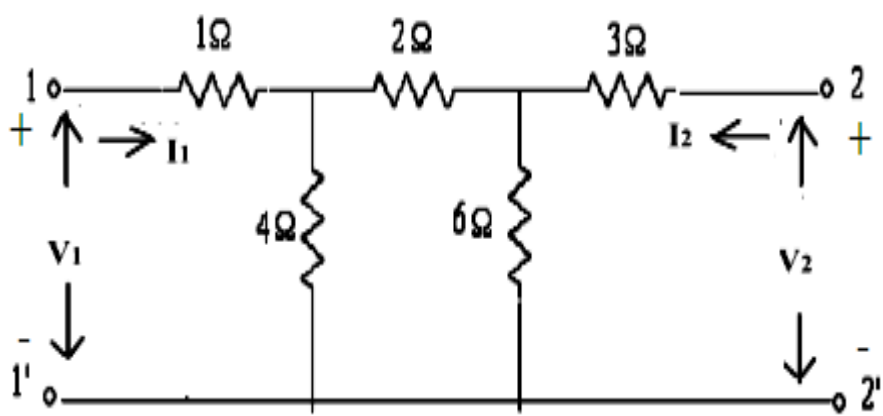8	<p>a) Obtain Z – parameters for the network shown below.</p> 	L4	CO3	7 M
---	---	----	-----	-----

	b)	Determine the y-parameters of the following network.	L4	CO3	7 M

UNIT-V

9	a)	Explain about parallel resonance with phasor diagrams.	L2	CO4	7 M
	b)	In a parallel resonant circuit shown in figure, find the resonant frequency, bandwidth, Q-factor and current at resonance.	L4	CO4	7 M

OR

10	a)	Obtain the expression for resonant frequency, bandwidth and Q-factor for series R-L-C circuit.	L3	CO4	7 M
	b)	Compare series resonance and parallel resonance.	L4	CO4	7 M