

Code: 20EE3301, 20EC3301

II B.Tech - I Semester – Regular Examinations - FEBRUARY 2022

ELECTRONIC DEVICES AND AMPLIFIER CIRCUITS
(Common for EEE, ECE)


Duration: 3 hours

Max. Marks: 70

Note: 1. This paper contains questions from 5 units of Syllabus. Each unit carries 14 marks and have an internal choice of Questions.
2. All parts of Question must be answered in one place.

UNIT – I

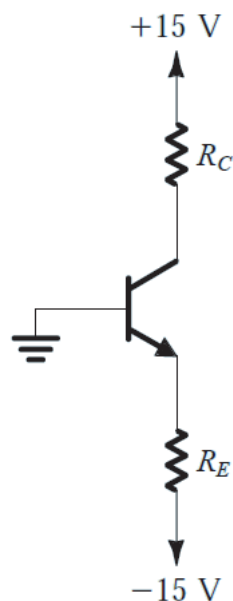1. a) With a circuit diagram, illustrate the operation of a common emitter amplifier and obtain its voltage gain expression. 7 M
- b) Design a circuit similar to that shown in below figure except that now the power supplies are $\pm 1.5V$ and the BJT has $\beta = 100$ and exhibits V_{BE} of $0.8V$ at $i_c = 1mA$. Design the circuit so that a current of 2 mA flows through the collector and a voltage of $+5V$ appears at the collector. 7 M



OR

2. a) Compare common base (CB), common emitter (CE) and common collector (CC) configuration of a transistor. For CE configuration prove that $I_C = \beta I_B + (\beta + 1) I_{CO}$ 7 M
- b) For a CE transistor amplifier circuit, $R_1 = 50K\Omega$, $R_2 = 25K\Omega$, $R_C = 10K\Omega$, $R_E = 10K\Omega$, $R_L = 30K\Omega$. Determine input and output impedances, current gain and voltage gain if transistor parameters are as follows $h_{ie} = 2K\Omega$, $h_{fe} = 100$, $h_{re} = 5 \times 10^{-4}$, $h_{oe} = 25\mu S$. 7 M

UNIT – II

3. a) Analyze the MOSFET biasing technique using a large drain-to-gate feedback resistance R_G . Design the drain-to-gate feedback biasing circuit to operate at a DC drain current of 0.5mA. Assume $V_{DD} = 5V$, $k_n' W/L = 1mA/V^2$, $\lambda = 0$. 7 M
- b) What are the main constructional differences between a MOSFET and a BJT? What effect do they have on the current conduction mechanism of a MOSFET? 7 M

OR

4. a) With neat diagram analyze the operation of MOSFET in depletion mode and derive its current equations. 7 M
- b) Differentiate between current voltage relationships of the N channel and P channel MOSFET. 7 M

UNIT-III

5. a) Obtain the expression for low frequency response of a MOSFET common source amplifier. 7 M

- b) A MOSFET is to operate at $I_D=0.1\text{mA}$ and is to have $g_m=1\text{mA/V}$. If $k_n=50\mu\text{A/V}^2$. Estimate the required W/L ratio and the overdrive voltage. 7 M

OR

6. a) Analyze the internal capacitances of a MOSFET and hence draw the high frequency model of MOSFET. 7 M
- b) Estimate the mid band gain A_M , and the upper 3-dB frequency f_H of a MOSFET CS amplifier fed with a signal source having an internal resistance $R_{sig}=100\text{k}\Omega$. The amplifier has $R_G=4.7\text{M}\Omega$, $R_D=R_L=15\text{k}\Omega$, $g_m=1\text{mA/V}$, $r_o=150\text{k}\Omega$, $C_{gs}=1\text{pF}$ and $C_{gd}=0.4\text{pF}$ 7 M

UNIT – IV

7. a) Explain the MOS differential pair with common mode input voltage and specify the input common mode voltage range. 7 M
- b) Show that if all transistors are operated at an overdrive voltage V_{ov} and have equal Early voltages $|V_A|$, the gain is given by $A_d = 2(V_A/V_{ov})^2$. Estimate the gain for $V_{ov}=0.25\text{V}$ and $V_A=20\text{V}$. 7 M

OR

8. a) Obtain input offset voltage of the MOS differential pair with necessary diagrams. 7 M
- b) An NMOS differential amplifier utilizes a bias current of $200\mu\text{A}$. The device have $V_t=0.8\text{V}$, $W=100\mu\text{m}$, and $L=1.6\mu\text{m}$, in a technology for which $\mu_n C_{ox}=90\mu\text{A/V}^2$. Find V_{GS} , g_m and the value of V_{id} for full-current switching. To what value should the bias current be changed in order to double the value of V_{id} for full- 7 M

current switching?

UNIT – V

9. a) Compare the operating regions of Bipolar and MOS transistors. 7 M
- b) Interpret the current steering circuit using five MOSFET transistors and distinguish the current source and current mirror. 7 M

OR

10. a) Explain the operation of MOS current steering circuit and mention its advantages. 7 M
- b) Show that for a MOSFET the selection of L and V_{ov} determines A_0 and f_T . In other words, show that A_0 and f_T will not depend on I_D and W . 7 M