

Code: 19EC3301

II B.Tech - I Semester – Regular Examinations – MARCH 2021**NETWORK THEORY AND ANALYSIS
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

-
- Note: 1. This question paper contains two Parts A and B.
 2. Part-A contains 5 short answer questions. Each Question carries 2 Marks.
 3. Part-B contains 5 essay questions with an internal choice from each unit. Each question carries 12 marks.
 4. All parts of Question paper must be answered in one place
-

PART – A

1. a) Find the average value of a cosine wave.
- b) Derive time constant in R-L circuit.
- c) Explain Maximum power transfer theorem.
- d) Define bandwidth and quality factor.
- e) Express h-parameters in terms of Z-parameters.

PART – B**UNIT – I**


2. a) A sine wave generator supplies a 500 Hz, 10 V, RMS signal to a 2 K Ω resistor in series with a 0.1 μ F capacitor. Determine the total impedance Z and current I. 6 M
- b) A sinusoidal voltage $v=50 \sin \omega t$ is applied to a series RL circuit. The current in the circuit is given by $i=25 \sin (\omega t-53^\circ)$. Determine apparent power, average power and power factor. 6 M

OR


3. a) A sine wave generator supplies a 50 Hz, 50 V, RMS signal to a series RLC circuit with $10\ \Omega$ resistor, $10\ \mu\text{F}$ capacitor and $0.5\ \text{H}$ inductor. Determine the total impedance Z and current I . 6 M
- b) Develop the phase relation between applied voltage and current for series RC excited by sinusoidal voltage and obtain the impedance. 6 M

UNIT – II

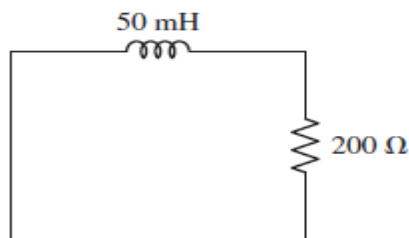4. a) If the inductor of Figure below has a current $i_L = 2\ \text{A}$ at $t = 0$, find an expression for $i_L(t)$ valid for $t > 0$, and its value at $t = 200\ \mu\text{s}$. 4 M




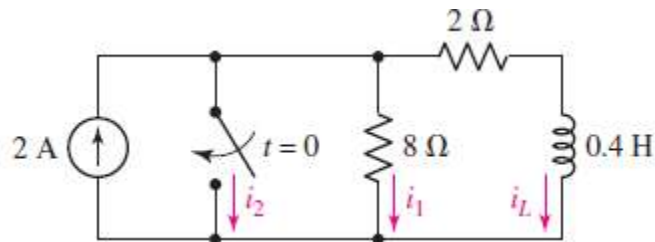- b) For the circuit of Figure below, find the value of 8 M
- (i) i_L ;
 - (ii) i_1 ;
 - (iii) i_2 . at $t = 0.15\text{s}$.



OR

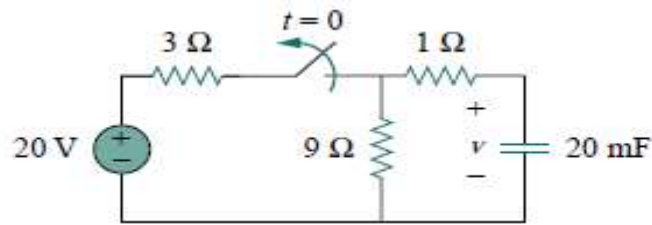
5. a) The switch in the circuit in Figure below has been closed for a long time, and it is opened at $t = 0$. Find $v(t)$ for $t \geq 0$. Calculate the initial energy stored in the capacitor. 6 M




- b) A series RC circuit is excited by DC voltage. Evaluate the expression for $i(t)$ when the switch is closed at $t=0$ and plot $i(t)$ vs. 't'. 6 M

UNIT-III

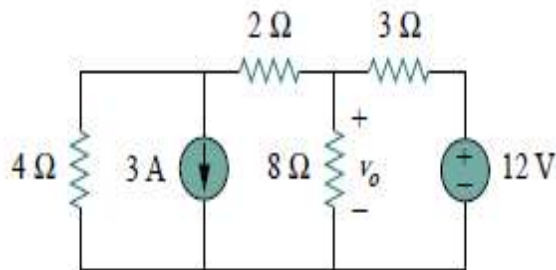6. a) Use source transformation to find V_o in the following circuit. 6 M




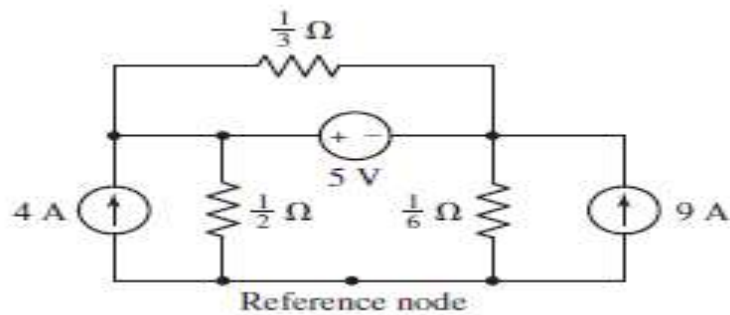- b) Compute the voltage across each resistor in the following figure. 6 M




OR

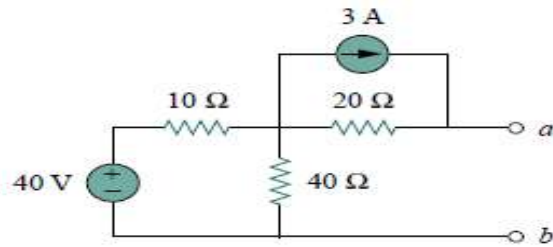7. a) Find the Thevenin's equivalent at terminals a-b of the circuit. 6 M




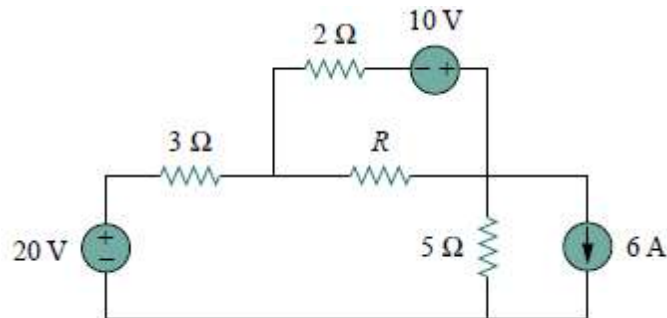- b) Find the maximum power that can be delivered to the resistor R in the circuit below 6 M



UNIT – IV

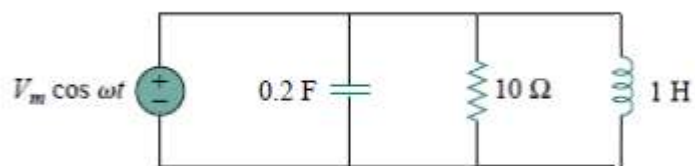8. a) Design a series RLC circuit that will have an impedance of 10Ω at the resonant frequency of $\omega_0 = 50 \text{ rad/s}$ and a quality factor of 80. Find the bandwidth. 6 M
- b) Calculate the resonant frequency of the circuit in Figure below. 6 M




OR


9. a) A series RLC network has $R = 2 \text{ k}\Omega$ & $L = 40 \text{ mH}$, and $C = 1 \text{ }\mu\text{F}$. Calculate the impedance at resonance and at one-fourth, one-half, twice, and four times the resonant frequency. 6 M
- b) A parallel resonant circuit with quality factor 120 has a resonant frequency of $6 \times 10^6 \text{ rad/s}$. Calculate the bandwidth and half-power frequencies. 6 M

UNIT – V

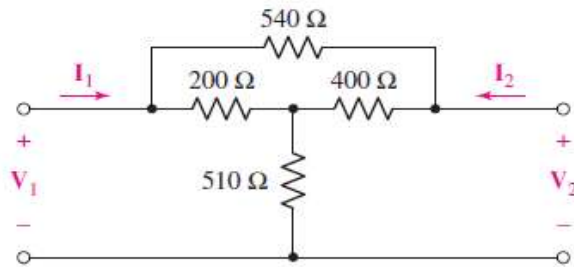10. a) Obtain a complete set of Y parameters to describe the two-port network as shown below. 6 M




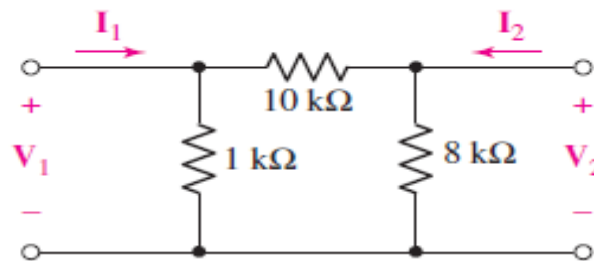- b) Obtain a complete set of h parameters which describe the two-port network as shown below. 6 M



OR

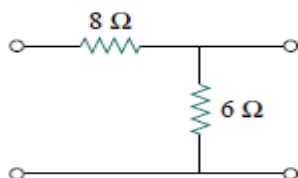11. a) Find the Z-Parameters for the below two port network. 4 M



b) Find the ABCD-Parameters for the below two port network. 8 M

