

Code: EC3T4

**II B.Tech - I Semester–Regular/Supplementary Examinations
November 2016**

**NETWORK ANALYSIS AND SYNTHESIS
(ELECTRONICS AND COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) State and explain Kirchhoff's laws.
- b) State the superposition theorem and write its importance.
- c) Explain the steps to apply Thevenin's Theorem.
- d) Define the terms network, graph, loop matrix.
- e) Write the properties of a tree in graph.
- f) Compare analysis and synthesis with respect to network.
- g) Write the relation between H-parameters and Y-parameters.
- h) Explain the parallel connection of two two-port networks.
- i) Briefly explain the concept of poles and zeros in a network.
- j) Write the steps to obtain the stability of a network function.
- k) Apply Routh Hurwitz criteria for the polynomial $P(s)=s^3+2s^2+4s+M$. "M" is adjustable.

PART – B

Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

2.

a) State and explain Tellegen's theorem. 8 M

b) Using compensation theorem, determine the ammeter reading when it is connected to 6Ω resistor as shown in fig. 1. The internal resistance of the ammeter is 2Ω . 8 M

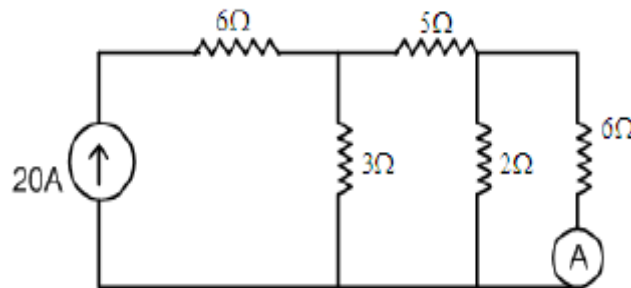


Fig. 1.

3.

a) For the resistive circuit in fig. 2, Determine the number of branches, number of nodes and number of links.

Write down the incident matrix and also develop equilibrium equation. 8 M

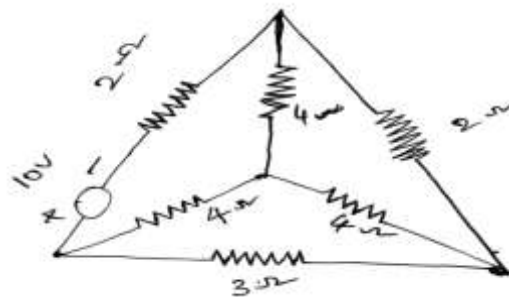


Fig. 2.

b) Derive the DC response of a series Resistor–Capacitor circuit. 8 M

4.

a) Find the y-parameters of the network shown in fig. 3 .

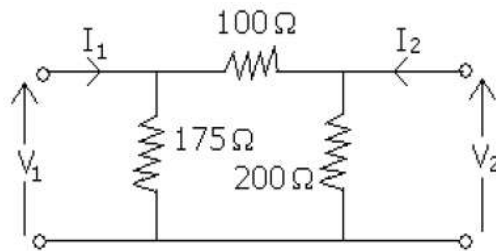


Fig. 3.

8 M

b) Calculate the Z-parameters for the lattice network shown in fig. 4. 8 M

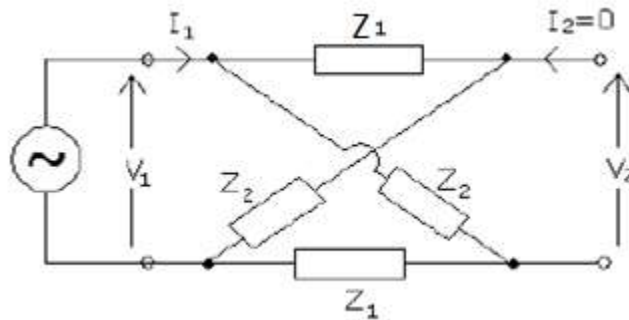


Fig. 4.

5.

a) Discuss the restrictions of location of poles and zeros in driving point functions. 8 M

- b) Determine the voltage transfer function v_2/v_1 for the fig. 5.

8 M

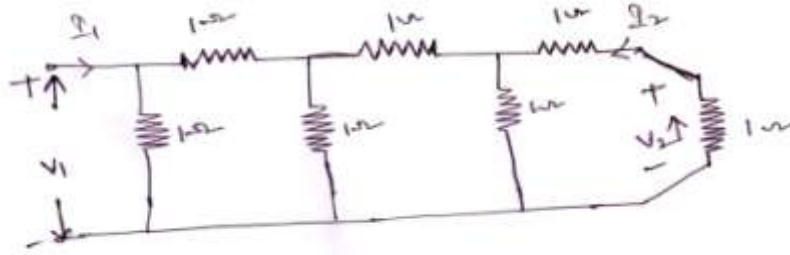


Fig.5.

6.

- a) Show the pole zero plot of the given network function $V(s)=10s / (s+3)(s+2)$ and obtain $v(t)$.

8 M

- b) What are the conditions specified by the Hurwitz polynomial? List the properties of Hurwitz polynomial.

8 M