

Code: EC3T4

**II B.Tech - I Semester–Regular/Supplementary Examinations  
November 2017**

**NETWORK ANALYSIS AND SYNTHESIS  
(ELECTRONICS & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

**PART – A**

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) State the maximum power transfer theorem.
- b) State Compensation Theorem.
- c) Referring to Figure-1, determine the thevenin equivalent of the network connected to  $R_L$

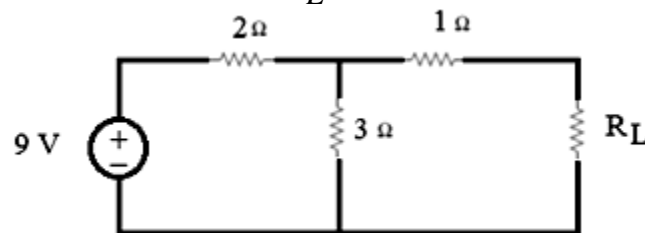


Figure-1

- d) Define Tie –set and Cut-set.
- e) In a source free RL circuit shown in Figure-2, the inductor has a current  $i_L = 2A$  at  $t=0$ , find an expression for  $i_L(t)$  valid for  $t > 0$ , and its value at  $t=200\mu s$

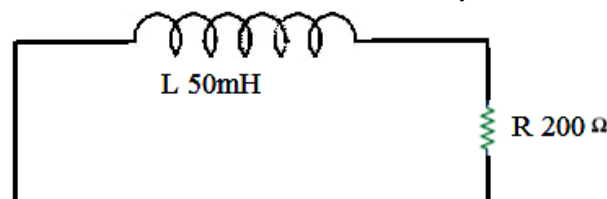


Figure-2

- f) Find the  $Y_{11}$  of a two port network, if the Z-Parameters of the same two port network are given by  $Z_{11} = 20\Omega$ ,  $Z_{12} = 10\Omega$ ,  $Z_{21} = 15\Omega$ ,  $Z_{22} = 5\Omega$ .
- g) Obtain the Z parameters for the network shown in Figure-3.

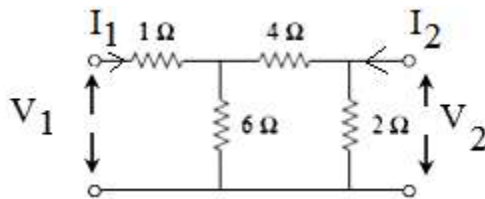


Figure-3

- h) Write the steps for realization of LC network functions.
- i) How do poles and zeros can be identified in circuit transfer function?
- j) Write the necessary and sufficient conditions for RC networks.
- k) Plot the pole – zero for the transfer function  $Y(S) = (2S^2 + S + 1) / (S^2 + S + 1)$

### PART – B

Answer any **THREE** questions. All questions carry equal marks.

3 x 16 = 48 M

2. a) For the circuit in Figure-4, use superposition theorem to determine the unknown branch current  $i_x$ . 8 M

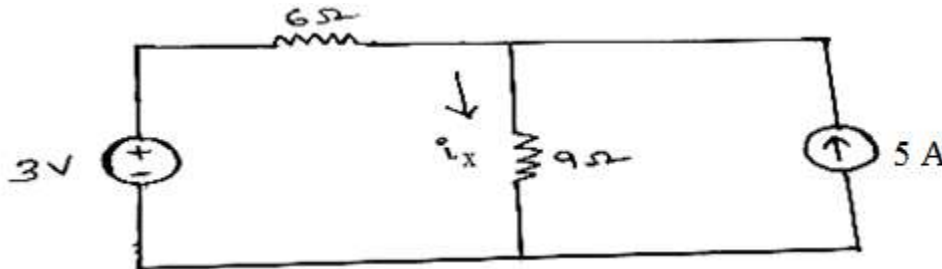


Figure-4

- b) Solve for the current in the 5 ohm resistor for the circuit shown in the Figure-5. 8 M

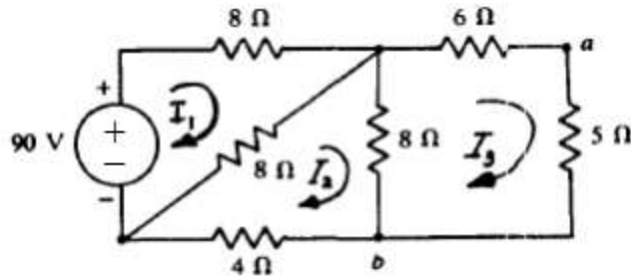


Figure-5

3. a) For the circuit in figure-6 obtain the dual circuit. 8 M

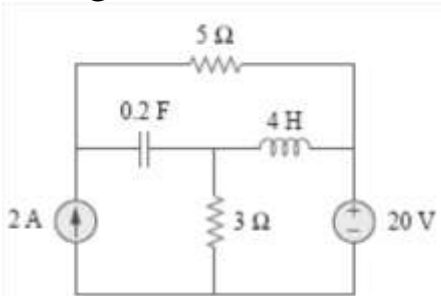


Figure-6

b) In the circuit shown in Figure-7. Find  $i_o$ ,  $v_o$  and  $i$  for all time, assuming that the switch was open for a long time.

8 M

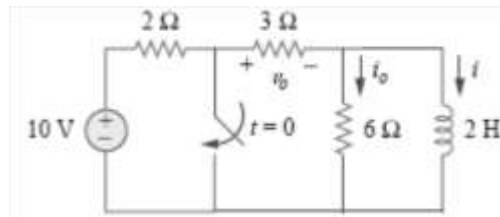


Figure-7

4. a) Obtain the h-Parameters for the network shown Figure-8.

8 M

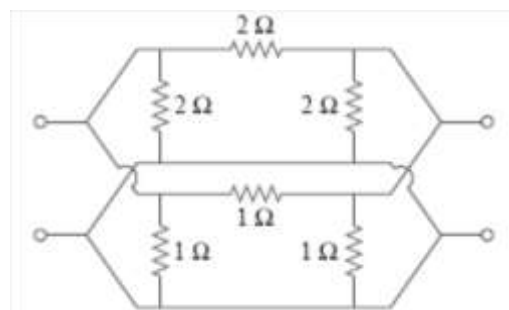


Figure-8

- b) Obtain the Y parameters for the T network as shown in Figure-9. 8 M

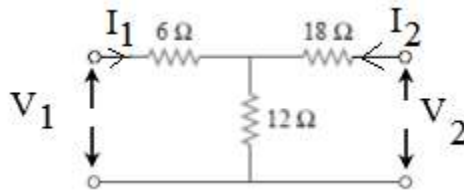


Figure-9

5. a) Determine the transfer function  $H(s) = V_o(s) / I_0(s)$  of the circuit shown in the Figure-10. 8 M

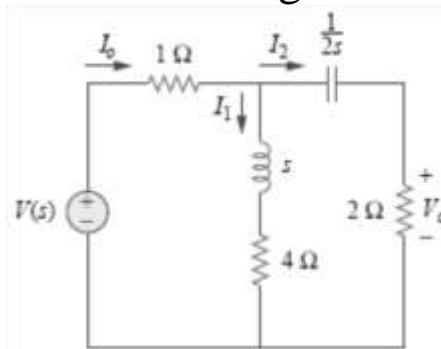


Figure-10

- b) Determine the poles and zeros of the impedance function  $Z(s)$  in the network shown in Figure-11. 8 M

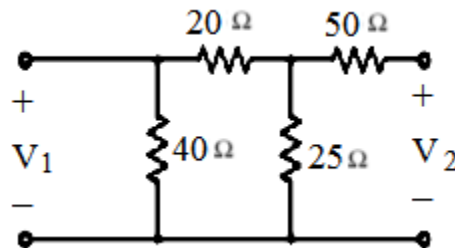


Figure-11

6. a) What are the conditions specified for the realization of RL functions? 8 M
- b) Synthesize the impedance function ,  $Z(s) = (S^3 + 3S) / (S^2 + 3)$ . 8 M