

Code: EC5T1

**III B.Tech - I Semester – Regular/Supplementary Examinations
MARCH 2021**

**LINEAR INTEGRATED CIRCUITS
(ELECTRONICS AND COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

PART – A

Answer *all* the questions. All questions carry equal marks

11x 2 = 22 M

1.

- a) What is the function of level translator?
- b) Draw the block diagram of Op-Amp.
- c) What are the limitations of ideal differentiator?
- d) List the applications of comparators.
- e) What is the function of all pass filter and draw the circuit diagram.
- f) List the advantages and disadvantages of switched capacitor filters.
- g) Draw the circuit diagram of Schmitt trigger using 555 timer.
- h) What is the difference between capture range and lock range in PLL?
- i) Draw the circuit diagram of 3-bit R-2R Ladder DAC.
- j) Define the terms Linearity and Resolution.
- k) What is the significance of Bode plots?

PART – B

Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

2. a) What do you mean by slew rate and derive an expression for slew rate for a voltage follower circuit using Op-Amp.

8 M

b) Explain about AC analysis of Dual input Balanced output Differential Amplifier.

8 M

3. a) Explain the Operation of Voltage to Current Converters using Op-Amp.

8 M

b) With a neat diagram derive the expression for frequency of oscillation for RC-Phase shift oscillator.

8 M

4. a) Design a first order low pass filter for the following specifications

i) Pass band voltage gain=2

ii) Cut-off frequency $f_c = 10 \text{ KHz}$.

Draw the frequency Response.

8 M

b) Derive the transfer function of 2nd order High pass filter using Op-Amp.

8 M

5. a) Explain the operation of 555 Timer as an astable multivibrator and derive an expression for time period of the output waveform. 8 M
- b) Discuss the following applications of Monostable mode using 555 timer.
- i) Missing pulse detector
 - ii) Linear ramp generator 8 M
6. a) Explain the operation of Successive Approximation ADC. 8 M
- b) Calculate the values of the LSB, MSB and full scale output for an 8-bit DAC for the 0 to 10V. 8 M