

Code: EE7T2

**IV B.Tech - I Semester – Regular / Supplementary Examinations  
MARCH - 2021**

**HVDC TRANSMISSION  
(ELECTRICAL & ELECTRONICS ENGINEERING)**

Duration: 3 hours

Max. Marks: 70

**PART – A**

Answer *all* the questions. All questions carry equal marks

11 x 2 = 22 M

1.

- a) Write advantages of HVDC transmission.
- b) Define transient reliability of HVDC system.
- c) Define pulse number of converter.
- d) Write importance of PIV calculation of HVDC converter.
- e) Define extinction angle of converter.
- f) List factors affecting converter control.
- g) Classify different HVDC converter faults.
- h) Write different sources of reactive power in HVDC system.
- i) Define Non-characteristic harmonic of HVDC converter.
- j) What is the purpose of filters in HVDC converters?
- k) List out startup procedure of HVDC link.

## PART – B

Answer any **THREE** questions. All questions carry equal marks.

$$3 \times 16 = 48 \text{ M}$$

2. a) Compare AC and DC transmission in Economical point of view. 8 M  
b) Explain planning for HVDC transmission. 8 M
3. Derive the expressions for output voltage and current of convertor by considering the effect of grid control and overlap less than  $60^\circ$  and obtain equivalent circuit. 16 M
4. List and describe about different firing angle schemes. 16 M
5. a) Explain the over current scheme employed in HVDC systems. 8 M  
b) Explain in detail about Misfire fault in HVDC. 8 M
6. a) Discuss the effect of increase in pulse number on current and voltage harmonics in HVDC converters. 8 M  
b) What are non-characteristic harmonics in HVDC systems? How are they generated? 8 M