

Code: 17EEPC1T1

I M.Tech-I Semester-Regular Examinations-February 2018

**ADVANCED COMPUTATIONAL METHODS IN  
POWER SYSTEMS  
(POWER SYSTEM & CONTROL)**

Duration: 3 hours

Max. Marks: 60

Answer the following questions.

1. a) Explain the following terms with examples

i) Incidence matrix 2 Mii) basic cut set matrix 2 Miii) basic loop 3 M

b) Obtain the oriented graph for the system shown in

Figure-1. Select any four possible trees. For a selected tree show the basic loops and basic cut-sets. 8 M

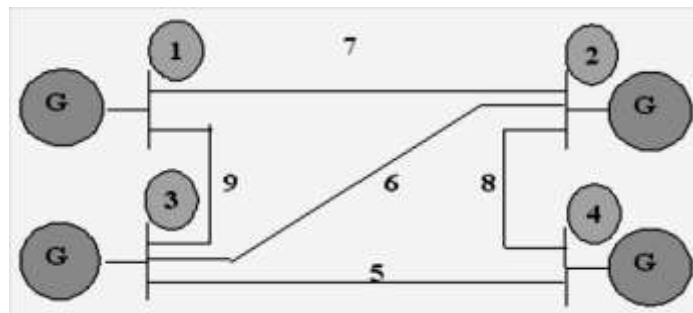


Figure-1

(OR)

2. a) Given that the self-impedances of the elements of a network referred by the bus incidence matrix given below are equal to:  $Z_1=Z_2=0.2$ ,  $Z_3=0.25$ ,  $Z_4=Z_5=0.1$  and


$Z_7=Z_6=0.4$  units, draw the corresponding oriented graph, and find the primitive network matrices. Neglect mutual values between the elements. 7 M

$\hat{A} =$

1	-1	0	0	0
1	0	-1	0	0
1	0	0	0	-1
0	0	0	-1	1
0	0	1	-1	0
0	1	-1	0	0
0	0	1	0	-1

b) Derive  $Y_{BUS}$  and  $Y_{BR}$  using singular transformation method. 8 M

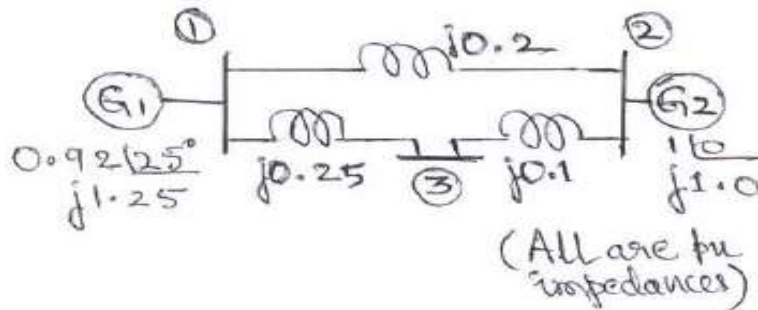3. a) Obtain  $Y_{BUS}$  for the impedance network shown in figure by the rule of inspection. 8 M



b) Derive the expression in polar form for the typical diagonal elements of the sub matrices of the Jacobian in NR method of load flow analysis. 7 M

(OR)

4. Explain with the help of a flow chart the computational procedure for load flow solution using G-S method, when all types of buses are included. 15 M

5. a) What are symmetrical faults? Explain their effect on power system. 7 M

b) A synchronous generator, rated 500 KVA, 440 Volts, 0.1 pu sub-transient reactance is supplying a passive load of 400 KW, at 0.8 power factor (lag). Calculate the initial symmetrical RMS current for a three-phase fault at the generator terminals. 8 M

**(OR)**

6. a) Describe the determination of symmetrical fault current using  $Z_{BUS}$  inversion. 7 M

b) A three phase 50 MVA, 11 kV generator is subjected to the various faults and the currents so obtained in each fault are: 2000 A for a three phase fault; 1800 A for a line-to-line fault and 2200 A for a line-to-ground fault. Find the sequence impedances of the generator. 8 M

7. a) Explain the procedural steps involved in  $Z_{bus}$  building algorithm for adding new bus to existing one. 7 M

b) Describe the procedural steps involved in  $Z_{bus}$  building algorithm for addition and removal of lines in power system. 8 M

**(OR)**

8. What is contingency analysis? Explain the contingency analysis for multiple line system. 15 M