

Code: 22ECMC2T6B

I M.Tech - II Semester – Regular Examinations - JULY - 2023**RF IC DESIGN
(MICROWAVE & COMMUNICATION ENGINEERING)**

Duration: 3 hours

Max. Marks: 60

Note: 1. This paper contains 4 questions from 4 units of Syllabus. Each unit carries 15 marks and have an internal choice of Questions.

2. All parts of Question must be answered in one place.

BL – Blooms Level

CO – Course Outcome

| | | | BL | CO | Max. Marks |
|----------------|----|--|----|-----|------------|
| UNIT-I | | | | | |
| 1 | a) | List any four RF applications and describe the steps for RF circuit design. | L2 | CO1 | 8 M |
| | b) | Explain sensitivity and dynamic range of the RF circuit. | L2 | CO1 | 7 M |
| OR | | | | | |
| 2 | a) | Describe the characteristics of passive IC components at RF frequencies. | L2 | CO1 | 7 M |
| | b) | Compare the characteristics of co-axial line and two -wire line. | L3 | CO1 | 8 M |
| UNIT-II | | | | | |
| 3 | a) | Explain bandwidth enhancement with fT doublers. | L2 | CO2 | 8 M |
| | b) | Describe the importance of current-reuse approach that helps in low-noise amplifier. | L2 | CO2 | 7 M |

| OR | | | | | | |
|-----------------|----|---|----|-----|------|--|
| 4 | a) | Explain power constrained noise optimization technique in low noise amplifier design. | L2 | CO2 | 8 M | |
| | b) | Discuss about linearity and large signal performance of LNA. | L2 | CO2 | 7 M | |
| UNIT-III | | | | | | |
| 5 | a) | Distinguish between different types of mixers. | L3 | CO3 | 6 M | |
| | b) | Draw and explain the super-heterodyne receiver block diagram and mention the importance of mixer in receiver. | L2 | CO3 | 9 M | |
| OR | | | | | | |
| 6 | a) | Describe the specifications of Mixer. | L2 | CO3 | 6 M | |
| | b) | Explain about diode-ring mixer with neat diagram. | L2 | CO3 | 9 M | |
| UNIT-IV | | | | | | |
| 7 | a) | Explain about RF synthesizer architecture. | L2 | CO4 | 10 M | |
| | b) | Differentiate static moduli and dithering moduli. | L3 | CO4 | 5 M | |
| OR | | | | | | |
| 8 | a) | Describe the importance of negative resistance oscillator and explain Simple differential negative resistance oscillator with neat diagram. | L2 | CO4 | 9 M | |
| | b) | Explain the effect of phase noise in RF communication. | L2 | CO4 | 6 M | |