

Code: EEPC2T4

**I M.Tech-II Semester-Regular Examinations-August 2014**

**ADVANCED POWER SYSTEM PROTECTION  
(POWER SYSTEM CONTROL AND AUTOMATION)**

Duration: 3 hours

Marks: 5x14=70

Answer any FIVE questions. All questions carry equal marks

- 1 a) Give the classification of protective schemes . 7 M
- b) Explain the principle of duality and prove it. 7 M
2. Explain different types of phase comparators with neat diagrams. 14 M
3. Explain about
  - a) IDMT relay. 7 M
  - b) Time current characteristics of over current relays . 7 M
- 4 a) Explain the effect of arc resistance ,power surges and line length on performance of distance relays. 7 M
- b) Describe with neat diagram static impedance relay . 7 M

- 5 a) Explain about carrier current protection. 7 M
- b) Describe the operational comparison of transfer trip and blocking schemes. 7 M
- 6 a) Write about the percentage differential protection in transformers . 7 M
- b) Write about frame leakage protection . 7 M
- 7 Write about microprocessor based distance relays . 14 M
- 8 a) Explain various schemes for the protection of travelling waves on transmission line. 7 M
- b) What is insulation coordination. Explain in detail. 7 M