

Code: **EEPC2T2**

**I M.Tech - II Semester-Regular Examinations – AUGUST 2016**

**FACTS CONTROLLERS  
(POWER SYSTEM CONTROL AND AUTOMATION)**

Duration: 3 hours

Max. Marks: 70

*Answer any FIVE questions. All questions carry equal marks*

1)

a) Discuss various FACTS controllers and their control attributes. 7 M

b) Explain the power flow and dynamic stability considerations of a transmission interconnection. 7 M

2)

a) Explain the working of a voltage source three level converters. 7 M

b) Explain the basic types of current source converters with their configurations. 7 M

3)

a) What are the objectives of static shunt compensators? 7 M

- b) Explain the functions of ideal midpoint reactive compensator in a two-machine power system. 7 M
- 4)
- a) Explain the working of TSC with relevant waveforms. 7 M
- b) Explain the functional control scheme for the FC-TCR. 7 M
- 5)
- a) Discuss the basic operating principle of switching type var generators. 7 M
- b) Obtain the basic block diagram of static compensators. 7 M
- 6)
- a) Explain with the help of a block diagram representation, how the STATCOM is implemented for the transient stability enhancement during a disturbance. 7 M
- b) What are the main components of complete control operation of a static compensators? Explain them. 7 M
- 7)
- a) Explain in detail, the basic operating control scheme of TSSC. 7 M

b) Discuss the functional system control scheme for the SSSC. 7 M

8)

a) Explain the basic operating principles of voltage source converters. 7 M

b) Explain the control characteristics of TSR. 7 M